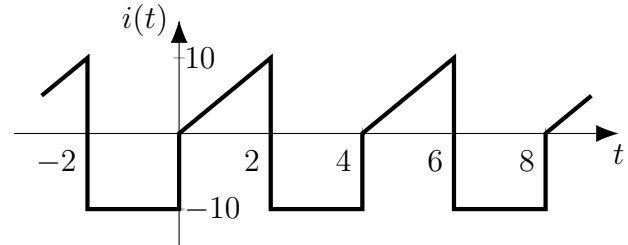


EE2015: Electric Circuits and Networks

Tutorial 9


(October 18, 2024)

- Consider the periodic signal shown on the right, which represents the current passing through a $10\ \Omega$ resistor.




- Find the RMS value of $i(t)$.
 - Find the average power absorbed by the resistor.
 - Find the value of the energy dissipated in the resistor over one cycle.
- A given circuit consists of a series combination of a sinusoidal voltage source $3 \cos(100t - 3^\circ)$ V, a $500\ \Omega$ resistor, a 30 mH inductor, and an unknown impedance. If it is observed that voltage source is delivering maximum power to the unknown impedance, what is its value?
 - If in the previous part, the 30 mH inductor is replaced by a $10\ \mu\text{F}$ capacitor, what is the value of the inductive component of the unknown impedance \mathbf{Z} if it is known that \mathbf{Z} is absorbing maximum power?

- Consider the network shown on the right. When \mathbf{X} is a $2.5\ \mu\text{F}$ capacitor, the voltage V_{AB} equals E_1 , where $E_1 = 100\text{ V}$. When \mathbf{X} is a 2 H inductor, V_{AB} equals $E_2 = 40\text{ V}$, and leads E_1 by 90° . Suppose now \mathbf{X} is replaced by a short-circuit. Find the current \mathbf{I}_{SC} flowing through AB under these conditions, and its phase angle with respect to E_1 .

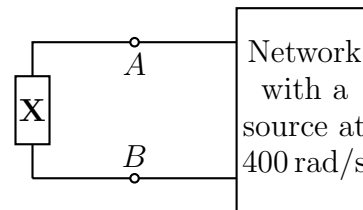

4.

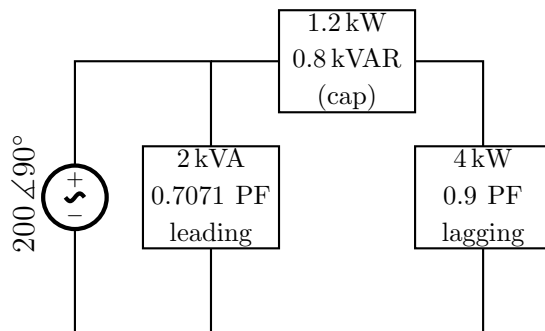

For the network shown on the left, calculate the following: (a) power factor, (b) average power, (c) reactive power, (d) apparent power, and (e) complex power delivered by the source.

- A sub-station operating at 50 Hz provides power to a large data center through a 20 km long high voltage line that can be modeled by a resistance of $5\ \Omega$ and an inductive

reactance of 20Ω . The voltage magnitude at the receiving end has to be maintained at 63.5 kV rms. If the consumer draws 20 MW of power at 0.707 lag power factor, find (i) line current (ii) active and reactive power absorbed by the line impedance (iii) the voltage and power factor at the sub-station end (iv) the active and reactive power at the sub-station end.

If a capacitor is connected directly across the load at customer side such that the receiving end current is at unity power factor with respect to receiving end voltage, recalculate the quantities (i)-(iv) for this case and the value of the capacitor.

Find the area of this capacitor, if we are planning to build a simple parallel plate capacitor with air as dielectric that can support 63.5 kV rms. Please note that breakdown field of air at atmospheric pressure is 30 kV/cm.