



EE2016 Microprocessor Theory & Lab

Aug – Nov 2024

Week3: Processor Design – ALU Components

Dr. R. Manivasakan, OSWM lab, IIT, Madras

Recap


- We have designed the memory from flip-flops and implemented MOV instruction
 - Connected flip-flops through single bit data bus
 - Connected group of flip-flops through multi-bit data bus
 - Register to register data transfer
 - MOV instruction
- We now design the ALU, how it is connected to data bus and how control signals are essential in its operation
- Reference: W. Stallings pages: 15, 18, 303, 305-347, 621-624, 674-676.

Arithmetic & Logic Unit (ALU)

- Does ALL the calculations / computations
 - } Arithmetic
 - Handles integers
 - May handle floating point (real) numbers
 - } Logical
 - } Core function which justifies the word “computer”
- Everything else in the computer is there to service this unit (apart from data flow)
- Advanced Arithmetic functions can be carried out
 - } Either by arithmetic routines / algorithms
 - } Or a separate FPU (maths co-processor)

Components of Arithmetic Logic Unit (ALU)




 
- Arithmetic Computing Engines
 - } Architectural (instruction)
 - Eg: ADD, MULT
 - } Organizational (Hardware)
 - Eg: Half & full adders, multipliers, Incrementors / decrementors,
- Logical Computing Engines
 - } Architectural (instructions)
 - AND, OR, Ex-OR, complements,
 - } Organizational (hardware)
 - Eg: Shifter (barrel shifter),
 - }



ALU Components



- ALU: Collection of functional units with common inputs and outputs with Output enable (Fn Select)

ALU - Multibit Arithmetic Operations

   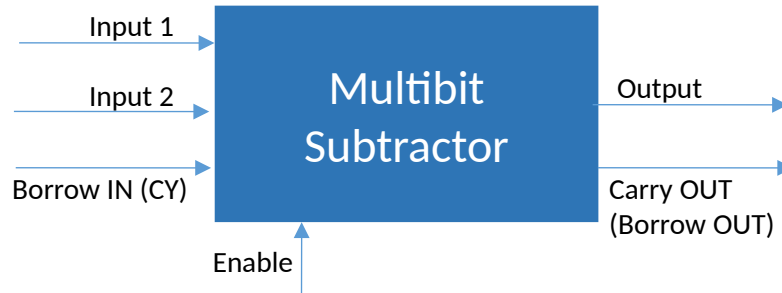


ALU Components

- Bitwise logical operation

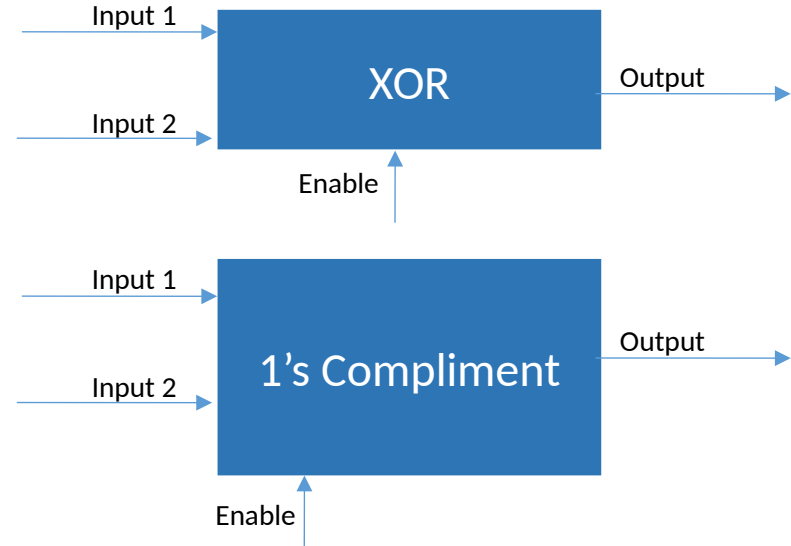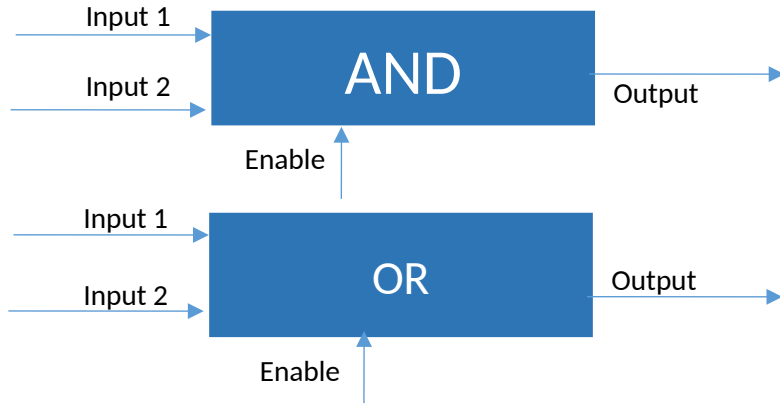


- Booth's Multiplier

 


Adders and Subtractors

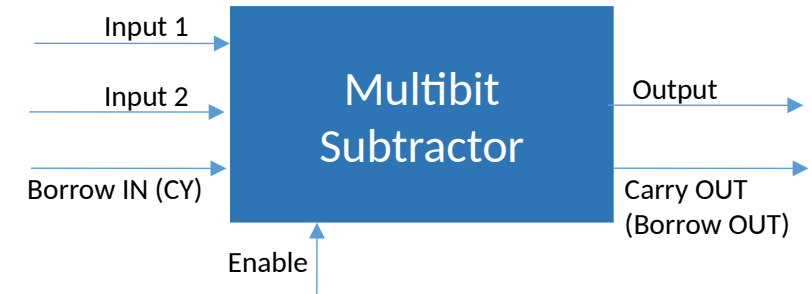- Combinational Logic can be used to design multi-bit parallel Adders and Subtractors
 - } Two multi-bit input words can be ADDED or subtracted giving an output word
 - } **Carry (CY) or Borrow (B) bits associated** with adders and subtractors respectively: denoted here as FLAG bits
- Similarly one can design multi-bit Logic functions, Comparators, Complement functions etc.




Hardware Realization of ALU

- Execution Unit (EU) consists of ALU & registers among others
 - › Registers are small memory units internal to EU
 - › to hold temporarily the operands apart from the intermediate results in a computation
 - › to hold the output and status of the result in a computation
 - › Hardware computational units (design choices):
 - › Design option #1: For every arithmetic & logical computations, design an exclusive hardware circuitry e.g. adder, comparator, XOR, subtractor, etc.
 - › Design option #2: Design a common combinational circuitry which implements each of the above operations with an option (through **function selection lines or control bits**) to **choose any one of them** at a time.
 - › In early 70's design option #2 was adopted in many commercial CPUs eg. ALU 74181
 - › Advantage is that a single circuitry is reused for all possible ALU operations --> optimizes hardware, reduces footprint etc.
- ALU **Function Select lines** enable one of these units to perform, at a time
 - › Input from and output to a set of pre-defined registers on the bus
 - › Flag register contain bits for CY, B, Comparator result (Y/N), Zero etc.

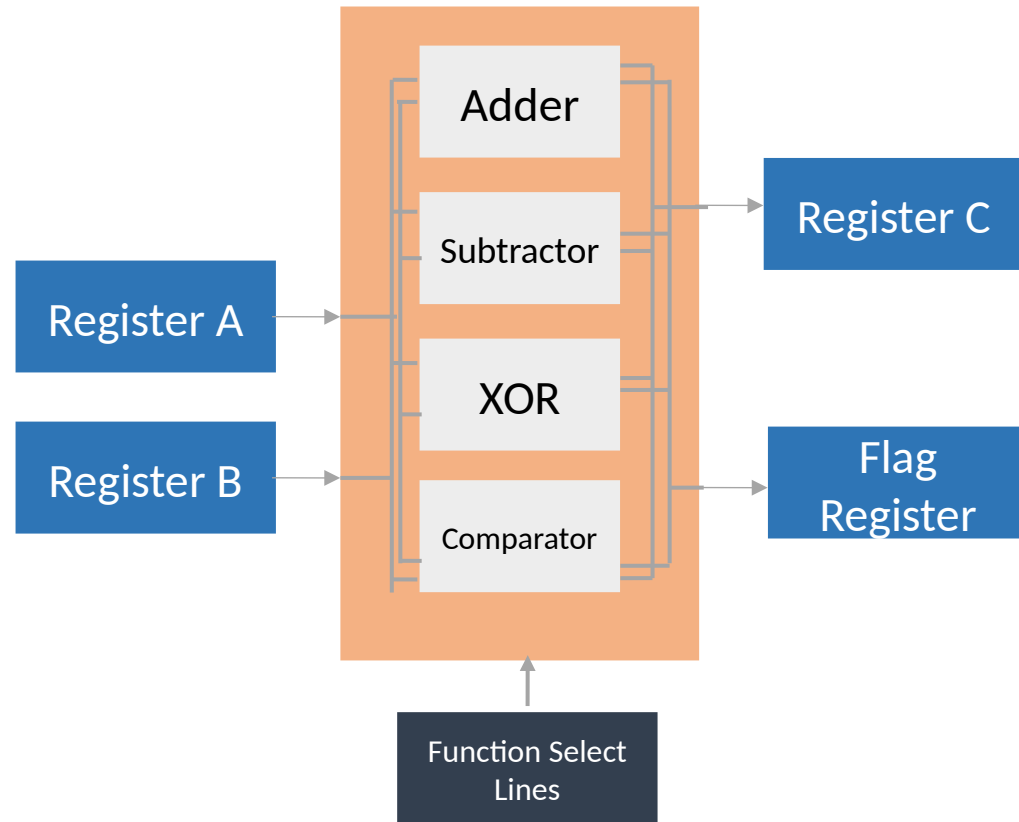

Hardware for Addition & Subtraction

 


OF = Overflow bit

SW = Switch (select addition or subtraction)

Unsigned Binary Multiplication

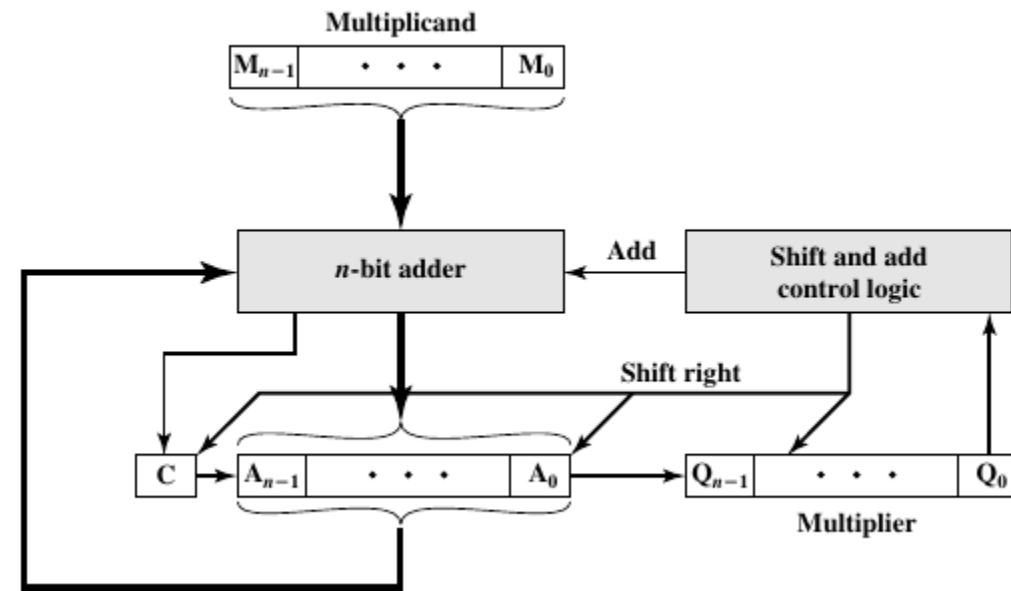
- Digital Circuit of Conventional Shift & Add Multiplier
- Improved version
 - Use of accumulator reduces memory space required
 - Save time in computation of partial products
 - 1 --> multiplicand
 - 0 --> zero
- Only unsigned binary multiplication



C	A	Q	M		
0	0000	1101	1011	Initial values	
0	1011	1101	1011	Add	} First cycle
0	0101	1110	1011	Shift	
0	0010	1111	1011	Shift	} Second cycle
0	1101	1111	1011	Add	
0	0110	1111	1011	Shift	} Third cycle
1	0001	1111	1011	Add	
0	1000	1111	1011	Shift	} Fourth cycle


Flow chart for unsigned binary multiplication

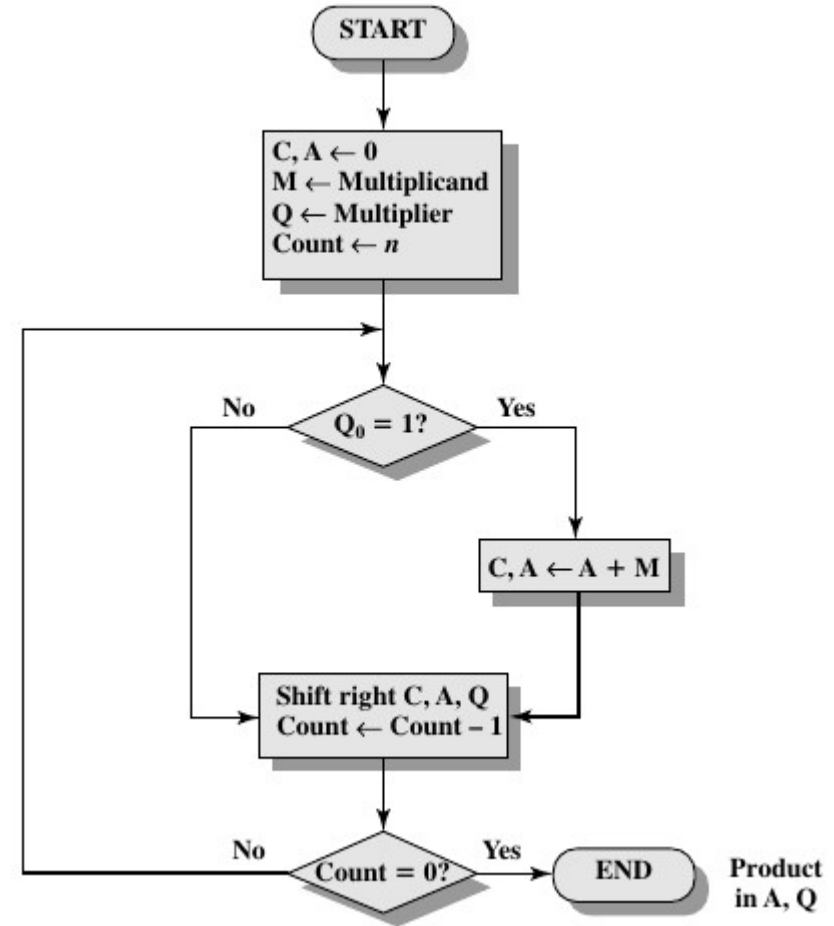- Flow chart for unsigned binary multiplication
 - } Only unsigned numbers
- Use of 2s compliment?
 - } Problems
 - } If both multiplicand and multiplier are negative
 - } Either of them negative --> fails
- S



Booth's Algorithm

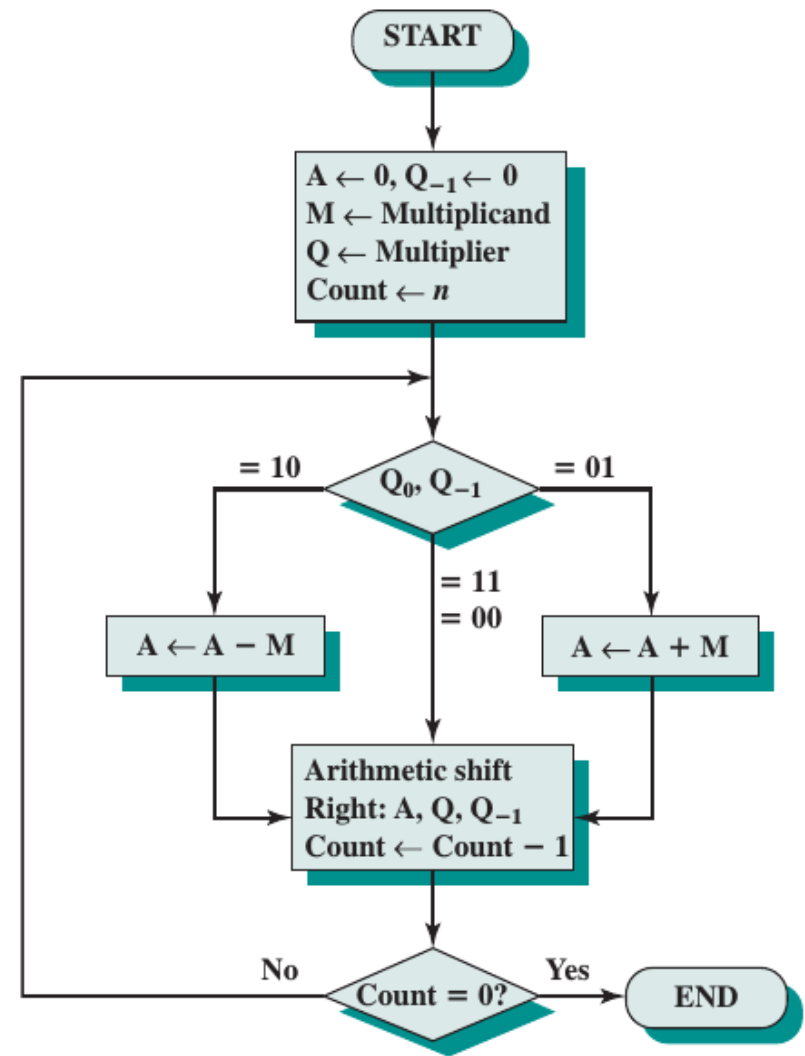- Booth's algorithm yields minimum number of computations (minimum computational overhead)
- S



Performance of Booth's Algorithm

- Given a multiplication problem, time taken to compute the product in various algorithms are compared
- S

S. No	Multiplier Algorithm	Delay time
1	Conventional Array	92 ns
2	Vedic	39 ns
3	QSD	33.891 ns
4	Modified Booth's algorithm	11.525 ns

Function Select Lines

- Each operation that an ALU can perform has a corresponding function line
 - } Number of function lines = number of arithmetic /logic operations that a processor can perform
- Each of these lines **activate one of the functional units** inside the ALU
 - } processor designer decides which function line triggers which operation
- Function lines activated/enabled by **control unit** of the processor

Function Line Number	Function
0	Add values in R1, R2
1	Increment value in R1
2	Compare Values in R1, R2
3	AND values in R1, R2
4	XOR values in R1, R2
5	Negate Value in R1
6	Subtract R1 from R2

Flag / Status Register

- A flag register or Condition Code Register is a collection of status flag bits giving information about the state of last operation performed (after operation)
 - } Different bits in register acts as a separate status indicators (defined by processor designer)
 - } **Flag bits can be used as input** in ALU operation (eg: Add with Carry) as well as input in an instruction (eg: Jump if Carry)

Flag Bit	Flag	Flag Name	Status Description
0	Z	Zero Flag	Indicates that the result of an arithmetic or logical operation (or, sometimes, a load) was zero.
1	C	Carry flag	Indicates whether carry was generated in previous addition
2	N	Negative flag	Indicates that the result of a mathematical operation is negative
3	V / O / W	Overflow flag	Indicates that the signed result of an operation is too large to fit in the register width using two's complement representation.

Mapped Registers

- Some processor registers mapped to serve a particular role for ALU
 - } **Mapped Input Registers**: These are the input registers that are mapped to act as the Inputs to the ALU functional units
 - } **Mapped Output Register**: Register that is used to always store the output of the ALU operation is called Mapped output register
 - } **Flag Register**: Similarly, a register that is used by ALU to reflect the flag values generated after performing an operation is called flag register
- These registers are hard wired to function as desired role
 - } The processor designer assigns these roles to the register
 - } Eg. R0, R1 -> Input registers, R2 -> Output register, R3 -> Flag Register
- **Modern processors dont have mapped registers (all general purpose registers (GPRs))**

4-bit ALU: 74181 integrated circuit

- The 74181


- } an evolutionary step between CPUs of the 1960s (discrete logic gates), and today's single-chip uP CPUs.
- } Although no longer used in commercial products, it is still referenced textbooks & technical papers.
- } Sometimes used in "hands-on" college courses for to train future computer architects.

- The 4-bit wide ALU can perform

- } add / subtract / decrement operations with or without carry, as well as AND / NAND, OR / NOR, XOR, and shift.
- } Multiply and divide functions are not provided

- ALU **Function Select lines** enable one of these units to perform specific operation

- } S0, S1, S2, S3
- } Ref: wiki

 


Function Table of 74181 4-bit ALU

Selection				Active-low inputs & outputs		Active-high inputs & outputs	
S3	S2	S1	S0	Logic (M = 1)	Arithmetic (M = 0) (Cn = 0)	Logic (M = 1)	Arithmetic (M = 0) (Cn = 1)
0	0	0	0	\overline{A}	A minus 1	\overline{A}	A
0	0	0	1	\overline{AB}	AB minus 1	$\overline{A + B}$	$A + B$
0	0	1	0	$\overline{A} + B$	$A\overline{B}$ minus 1	\overline{AB}	$A + \overline{B}$
0	0	1	1	Logical 1	-1	Logical 0	-1
0	1	0	0	$\overline{A + B}$	A plus ($A + \overline{B}$)	\overline{AB}	A plus ($A\overline{B}$)
0	1	0	1	\overline{B}	AB plus ($A + \overline{B}$)	\overline{B}	($A + B$) plus ($A\overline{B}$)
0	1	1	0	$\overline{A \oplus B}$	A minus B minus 1	$A \oplus B$	A minus B
0	1	1	1	$A + \overline{B}$	$A + \overline{B}$	$A\overline{B}$	$A\overline{B}$ minus 1
1	0	0	0	\overline{AB}	A plus ($A + B$)	$\overline{A} + B$	A plus AB
1	0	0	1	$A \oplus B$	A plus B	$\overline{A \oplus B}$	A plus B
1	0	1	0	B	$A\overline{B}(A + B)$	B	($A + \overline{B}$) plus AB
1	0	1	1	$A + B$	$A + B$	AB	AB minus 1
1	1	0	0	Logical 0	A plus A	Logical 1	A plus A
1	1	0	1	$A\overline{B}$	AB plus A	$A + \overline{B}$	($A + B$) plus A
1	1	1	0	AB	$A\overline{B}$ plus A	$A + B$	($A + \overline{B}$) plus A
1	1	1	1	A	A	A	A minus 1

Engines in Execution Unit: Generic Model

- Load & Store Unit
 - In LSA architecture, instructions exclusively do either memory or ALU operations
 - No ALU operations possible directly on operands from main memory, in LSA
 - The load-store unit (LSU) usually includes a queue which acts as a waiting area for memory instructions, and the unit itself operates independently of other processor units.
- Internal General Purpose Registers (GPRs)
 - Within EU, faster & scratchpad purpose.
- Special Function Registers (SFRs)
 - PC (Program Counters), SP (Stack Pointers), LR (Link Register), SR (Status Registers)
- Booths Multiplier
 - Multiplies two signed 2's complement numbers
 - Overall number of computations (binary additions, subtractions, shift operations) in Booths algorithm are less than that of conventional multiply-shift-add algorithm --> faster
- Incrementor/ Decrementer
 - Incrementer / Decrementer is used for calculating memory addresses, particularly for array indexing or sequential data access
 - PC update, loop control (eg analogous to “for” loops),
 - Pointer manipulations (increment / decrement pointer values)
- Flag Registers
 - Result of arithmetic and logical operation in EU is often accompanied by events (flags) which are used in furtherance of calculations
 - Typical flags are: Negative (N), Zero (Z), Sign (S), Carry (C)
- Floating Point Unit
 - Computations of all of floating point arithmetic

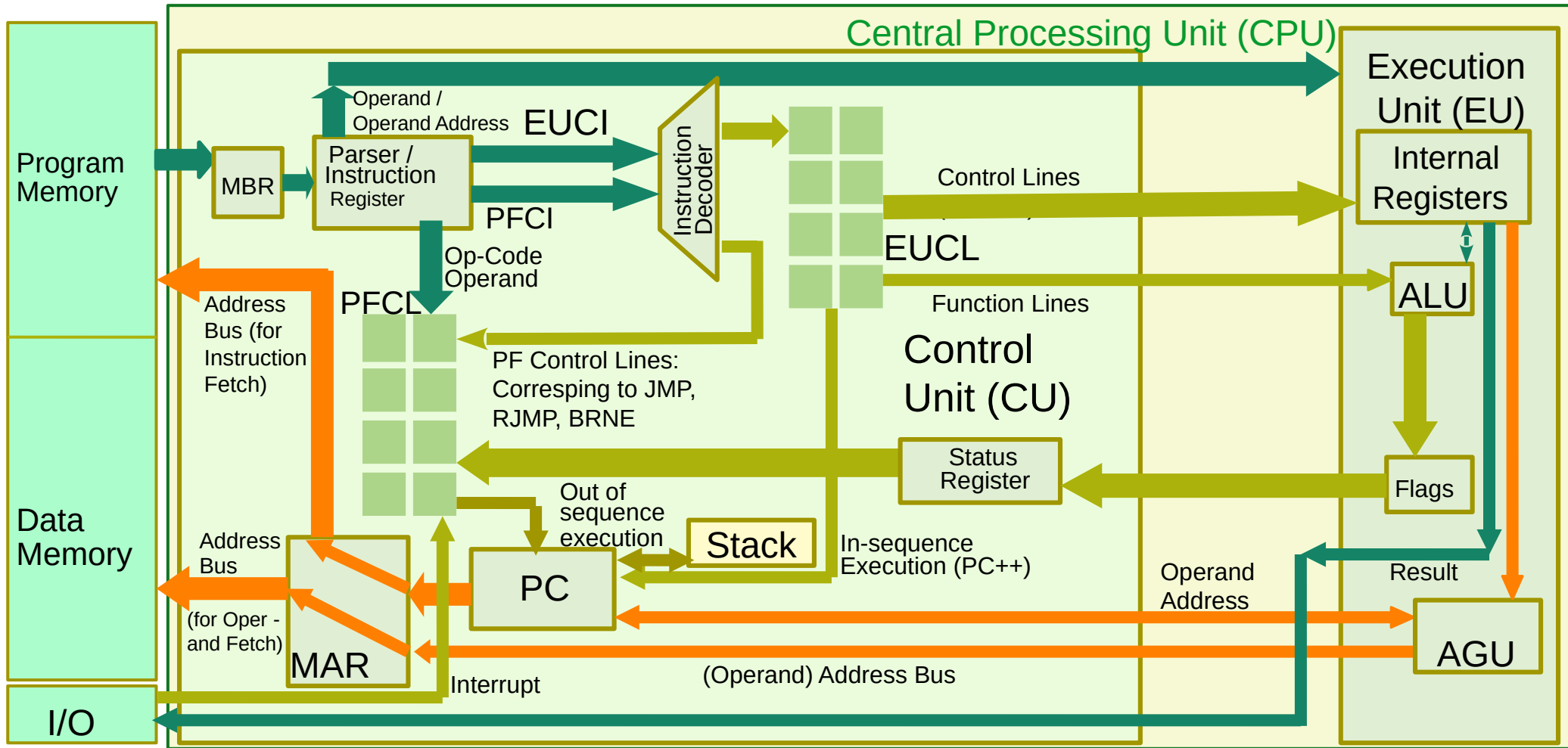


Putting CU Together: Control Unit

- Memory Buffer Register (MBR)
 - › Memory which stores temporarily the instruction to be executed, currently
- Memory Address Register (MAR)
 - › Register which contains the address of the operand to be fetched
- Instruction Register (or Instruction Decoder)
 - › Decodes the given OP code and generates hardware level signals to execute the corresponding command
- (Call) Stack & Stack Pointer
 - › Special memory area (stack data structure), wherein the information about the active subroutines are stored.
- Program Counter (PC)
 - › Instruction pointer – points to the next instruction to be executed
- Other Internal registers in CU
 - › Flag register (eg. CPSR) and status registers (eg. Program Status Word)


Putting CU Together: Control Unit

- Execution Unit Control Logic (EUCL):
 - } generates the necessary control signals (once the instruction is decoded) that activate specific functional units within the EU.
 - } The above control signals coordinate the activities of the ALU, registers, shifters, AGC & other components to execute the instruction correctly.
 - } manages the allocation of hardware resources within the EU to ensure that the instruction can be executed without conflicts – eg. ensure that registers are available for reading and writing, that the ALU is free for the required operation, and that data paths are correctly configured.
 - } coordinates the timing and synchronization of operations within the EU, ensuring that instructions are executed in the correct sequence and that results are available when needed.
- Program Flow Control Logic (PFCL):
 - } responsible for coordinating and controlling the operations, including decoding and executing PFCI instructions
 - } handles control flow instructions, such as branches & (conditional) jumps.
 - } manages conditional execution instructions, evaluates condition flags or values to decide whether to execute the instruction or skip it - essential for implementing conditional branching
 - } determines the new program counter (PC) value to specify the address of the next instruction to be executed, during branches & (conditional) jumps.

AVR Microcontrollers

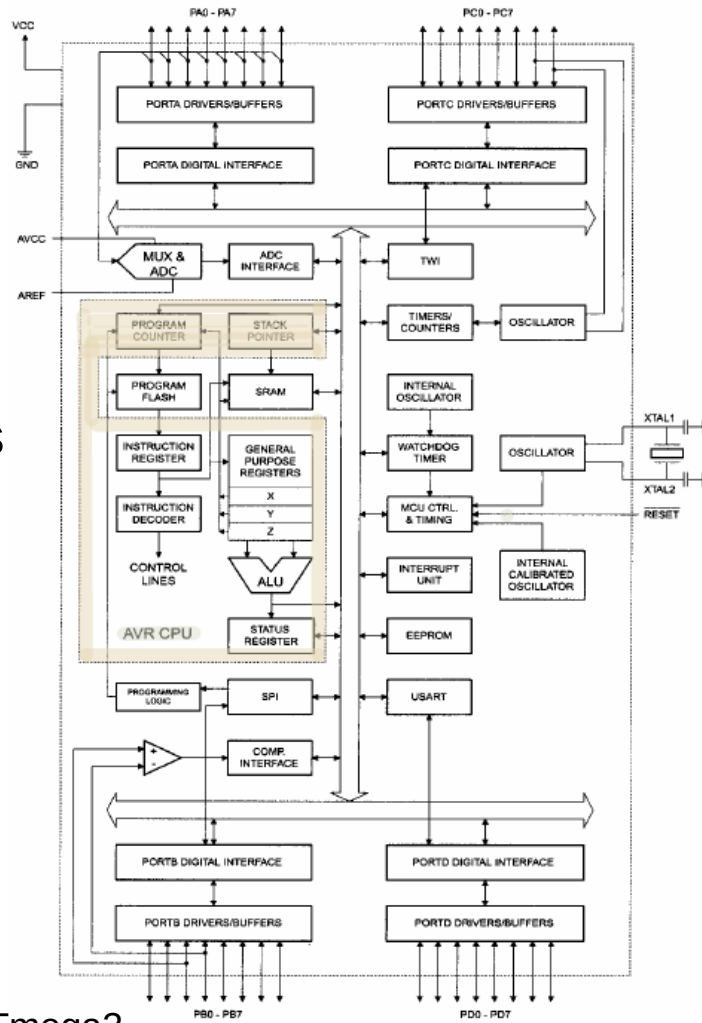

ATmega328P

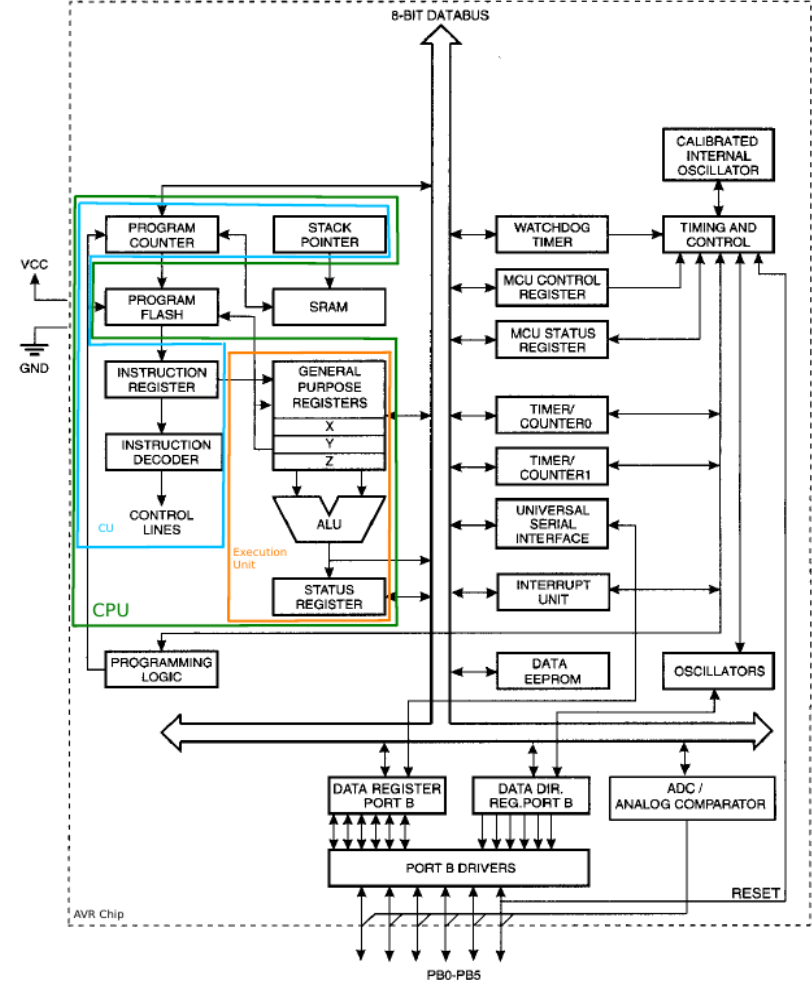

ATtiny25