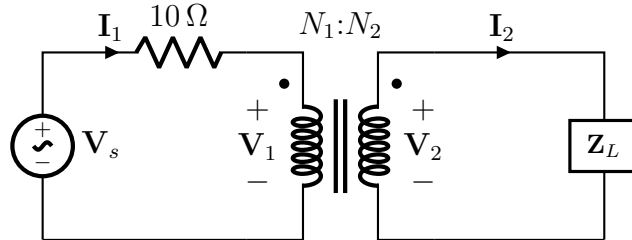


# EE2015: Electric Circuits and Networks

## Tutorial 10

(November 4-5, 2024)


- Let  $N_1 = 1000$  turns and  $N_2 = 5000$  turns in the ideal transformer shown on the right. If  $\mathbf{Z}_L = 500 - j400 \Omega$ , i) find the average power delivered to  $\mathbf{Z}_L$  in each of the following two cases:




- $\mathbf{I}_2 = 1.4 \angle 20^\circ \text{ A rms}$ , (b)  $\mathbf{V}_1 = 80 \angle 100^\circ \text{ V}$

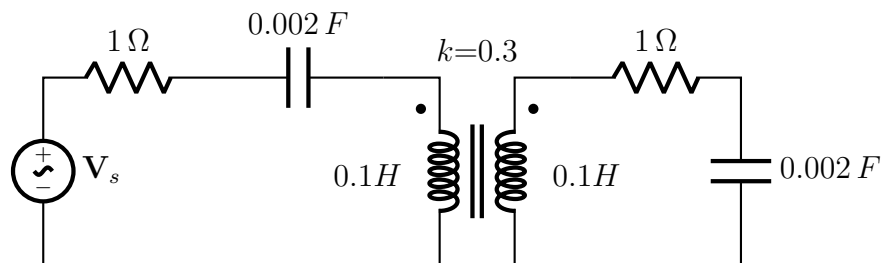ii) For  $\mathbf{V}_1 = 80 \angle 100^\circ \text{ V}$ , find:


- The primary side equivalent circuit that incorporates the reflected secondary side load impedance.
  - The secondary side equivalent circuit that incorporates the reflected primary side source impedance.
- Find  $\omega$  for which the impedance seen by the input source is purely resistive?



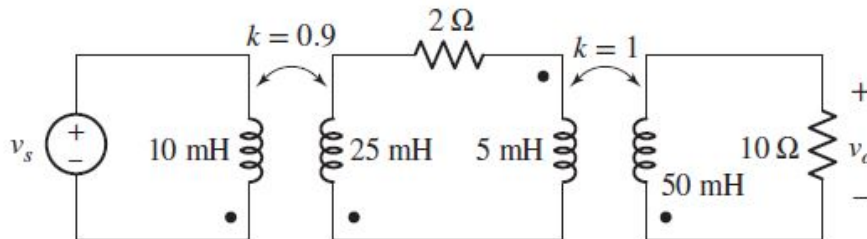- For the circuit below, find the equivalent 2-port Transmission parameters. Calculate  $v_o$  for the case where  $v_s = 12 \sin 500t \text{ V}$ .



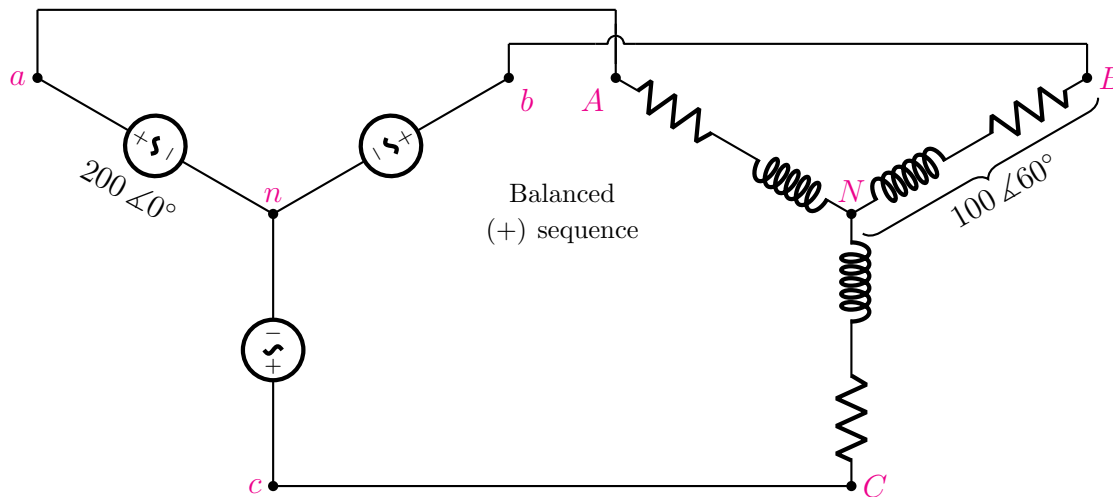4. For the three-phase circuit shown below, find the phase and line currents, and the phase and line voltages. What is the total power dissipated in the three-phase load? Assume that the line resistance is negligible.



5. A balanced three-phase three-wire system supplies power to a balanced Y-connected load. Assume that the line resistance is negligible. Each phase contains three loads in parallel, viz.,  $-j100 \Omega$ ,  $100 \Omega$ , and  $50 + j50 \Omega$ . Assume a positive phase sequence with  $\mathbf{V}_{ab} = 400 \angle 0^\circ \text{ V}$ . Find (a)  $\mathbf{V}_{an}$ , (b)  $\mathbf{I}_{aA}$ , and (c) total power drawn by the load.
6. A balanced  $\Delta$ -connected load with phase impedance of  $23.7 + j17.1 \Omega$  at 50 Hz is supplied from a 400 V, 50 Hz balanced Y-connected source through a line with impedance of  $0.1 + j0.3 \Omega$  in each line. Find (i) the line current and load voltage, (ii) the load-branch currents and (iii) the active and reactive power delivered by the source and delivered to the load. Redo the calculations by converting the  $\Delta$ -connected load to its equivalent Y-connected load.
7. A balanced three-phase three-wire supply is terminated with two  $\Delta$ -connected loads in parallel. Assume that the line resistance is negligible. Load 1 draws 40 kVA at a lagging PF of 0.8 while Load 2 absorbs 24 kW at a leading PF of 0.9. Let  $\mathbf{V}_{ab} = 440 \angle 30^\circ \text{ V}$ . Furthermore, assume that the line resistance is zero. Calculate the following quantities: (a) phase current  $\mathbf{I}_{AB}^{(1)}$  for the lagging load, (b)  $\mathbf{I}_{AB}^{(2)}$ , (c)  $\mathbf{I}_{aA}$ , and (d) total power drawn by the loads.
8. A balanced three-phase system with a line voltage of 400 V is connected to a balanced  $\Delta$ -connected load. Assume that the line resistance is negligible. Calculate the line current and per-phase load impedance if the load draws, (a) 1 kW at a lagging PF of 0.85, and (b) 300 W per phase at a leading PF of 0.92.