

# EC2015 Electric Circuits and Networks – Tutorial 1 Solutions

August 9th, 2024

1.


$$V_{8\Omega} = 2 \times 8 = 16V$$

Applying KVL in loop A,

$$30 - 16 - V_1 = 0$$

$$\Rightarrow V_1 = 14V$$
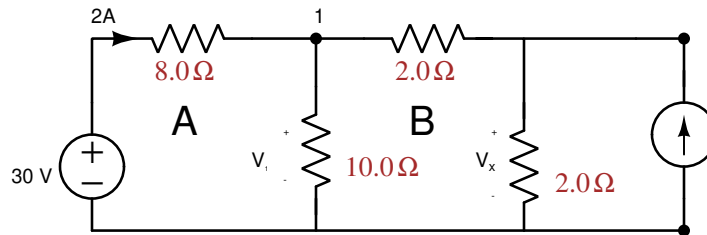
$$\Rightarrow I_{10\Omega} = \frac{14}{10} = 1.4A$$



Applying KCL at node 1,

$$I_{8\Omega} = I_{2\Omega} + I_{10\Omega}$$

$$\Rightarrow I_{2\Omega} = 0.6A$$

Applying KVL in loop B,

$$V_{10\Omega} - V_{2\Omega} - V_x = 0$$

$$\Rightarrow V_x = 14 - 1.2 = 12.8V$$

2.  $i(t) = \cos \omega_1 t + 2 \cos \omega_2 t$

a)  $v(t) = 10i(t) = 10 \cos \omega_1 t + 20 \cos \omega_2 t$

$\therefore \omega_1, \omega_2$  are the frequency components present in  $v(t)$  .

b)  $v(t) = 10i(t) + 0.1i^2(t)$

$$v(t) = 10(\cos \omega_1 t + 2 \cos \omega_2 t) + 0.1(\cos \omega_1 t + 2 \cos \omega_2 t)^2$$

$$= 10(\cos \omega_1 t + 2 \cos \omega_2 t) + 0.1 \left[ \cos^2 \omega_1 t + 4 \cos^2 \omega_2 t + 4 \cos \omega_1 t \cos \omega_2 t \right]$$

$$= 10(\cos \omega_1 t + 2 \cos \omega_2 t) + 0.1 \left[ \frac{1 + \cos 2\omega_1 t}{2} + 2(1 + \cos 2\omega_2 t) + 2 \cos(\omega_1 + \omega_2)t + 2 \cos(\omega_1 - \omega_2)t \right]$$

$$= 0.25 + 10(\cos \omega_1 t + 2 \cos \omega_2 t) + 0.1 \left[ \frac{\cos 2\omega_1 t}{2} + 2 \cos \omega_2 t + 2 \cos(\omega_1 + \omega_2)t + 2 \cos(\omega_1 - \omega_2)t \right]$$

$\therefore$  the frequency components in  $v(t)$  are:  $0, \omega_1, \omega_2, 2\omega_1, 2\omega_2, \omega_1 + \omega_2, \omega_1 - \omega_2$

3. The input, switch and the output waveforms are given below:

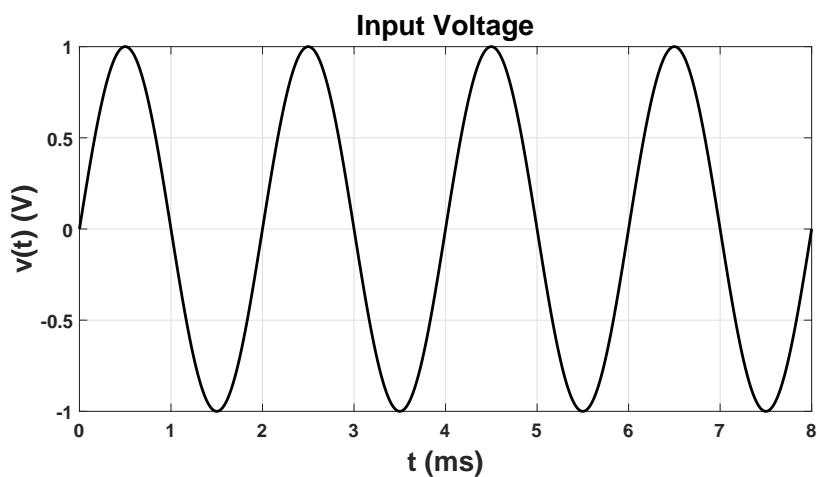


Figure 1

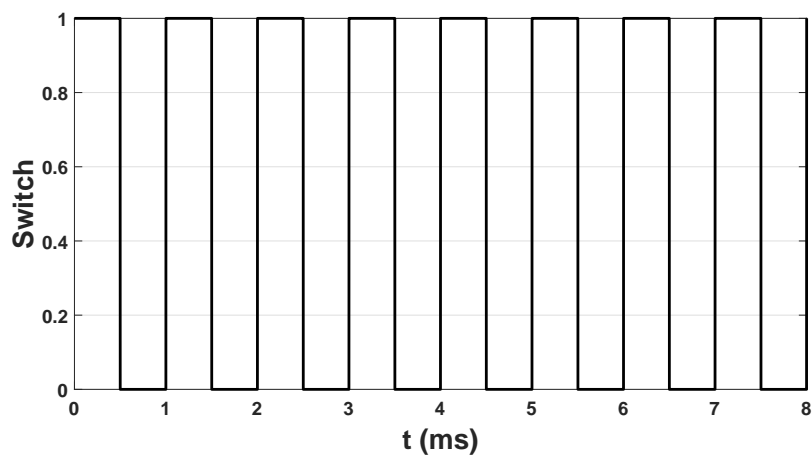


Figure 2

When switch is closed,

$$i(t) = \frac{1}{10} \sin(1000\pi t)$$

When switch is open,

$$i(t) = \frac{1}{20} \sin(1000\pi t)$$

Therefore  $i(t) = \sin(1000\pi t)f(t)$ , where  $f(t)$  is a square wave oscillating between 0.05 and 0.1.

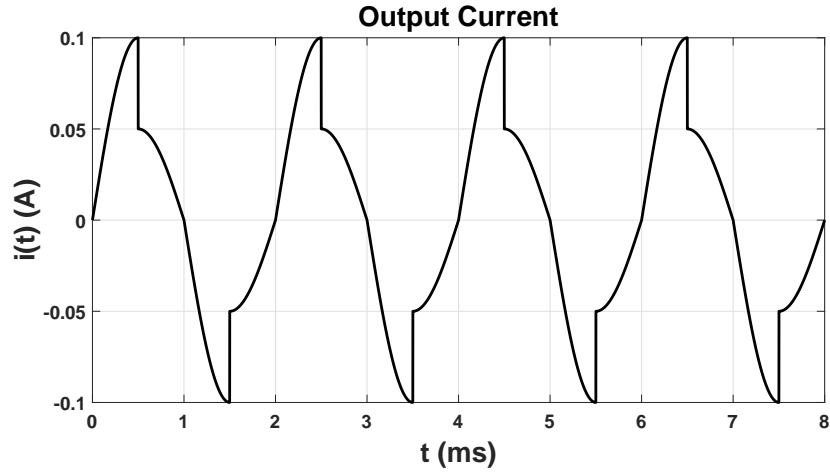


Figure 3

$f(t)$  can be expanded as a Fourier series. Since it is a square wave, it will have only odd harmonics. Therefore the frequencies present in the output are  $500 \pm k1000$  Hz and  $-500 \pm k1000$  Hz,  $k$  odd

The system is linear (output scales with input), but time variant.

4. (a)  $f(t) = u(t) - 2u(t - 2)$

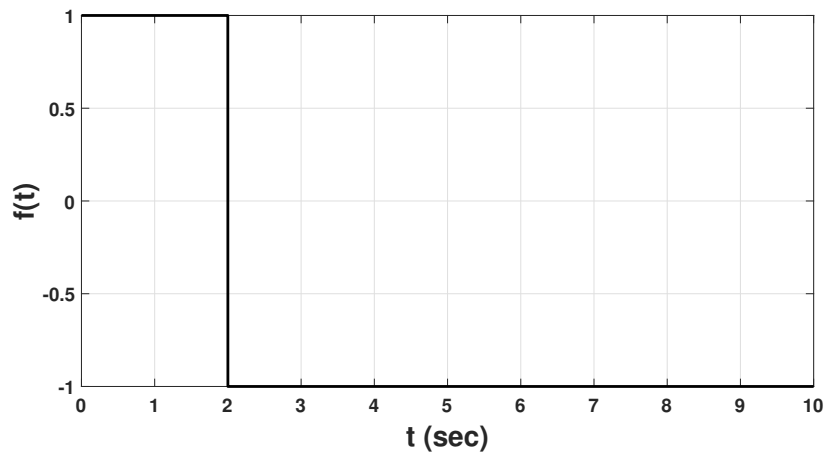


Figure 4

- (b)  $f(t) = \delta(t) - 2\delta(t - 1) + \delta(t - 2)$

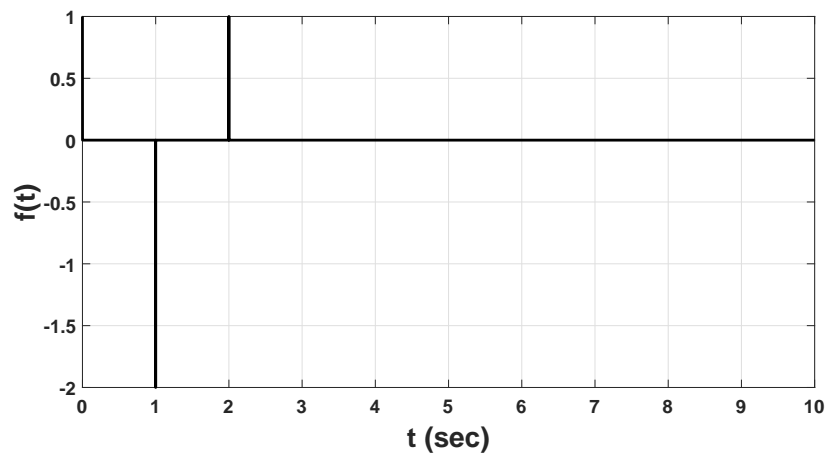


Figure 5

(c)  $f(t) = e^{-2t}u(t)$

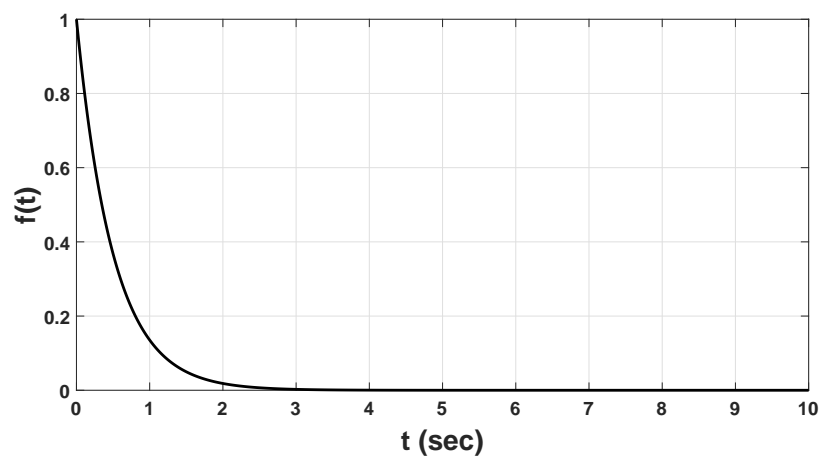


Figure 6

(d)  $f(t) = \cos(t)u(t)$

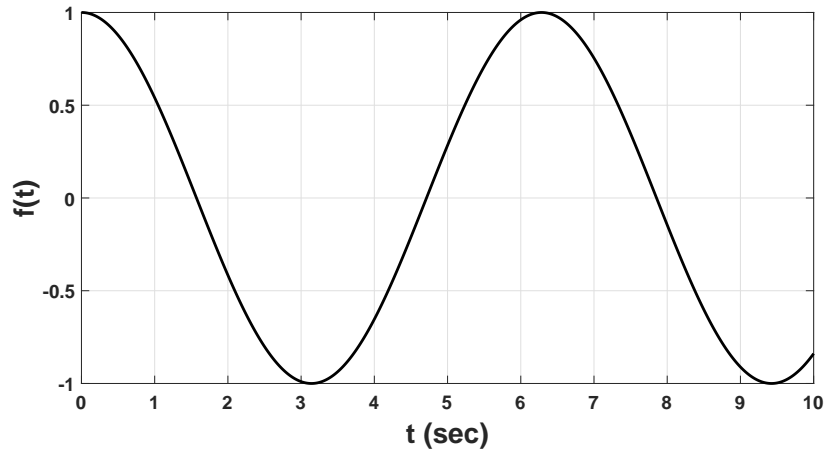


Figure 7

5. For zero initial conditions,

$$\text{Capacitor voltage, } V_C(t) = \frac{1}{C} \int i(t) dt = \int i(t) dt \quad (C=1F)$$

$$\text{Inductor voltage, } V_L(t) = L \frac{di(t)}{dt} = \frac{di(t)}{dt} \quad (L=1H)$$

$$(a) \quad i(t) = u(t) - 2u(t-2)$$

$$V_C(t) = tu(t) - 2(t-2)u(t-2)$$

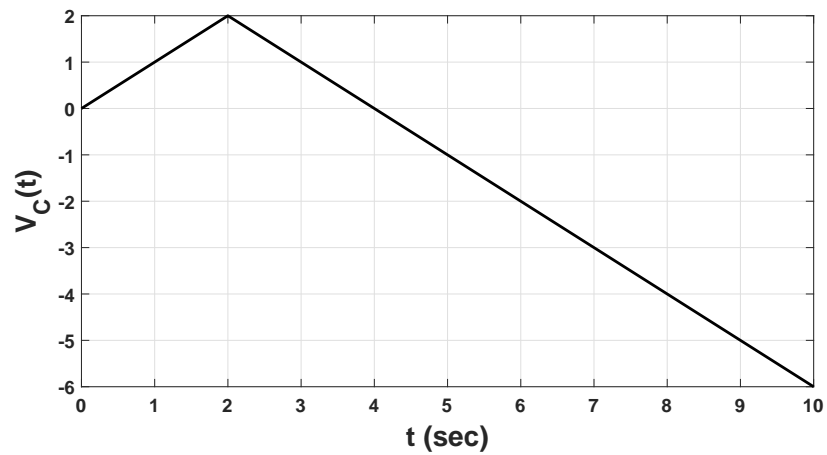


Figure 8

$$V_L(t) = \delta(t) - 2\delta(t-2)$$

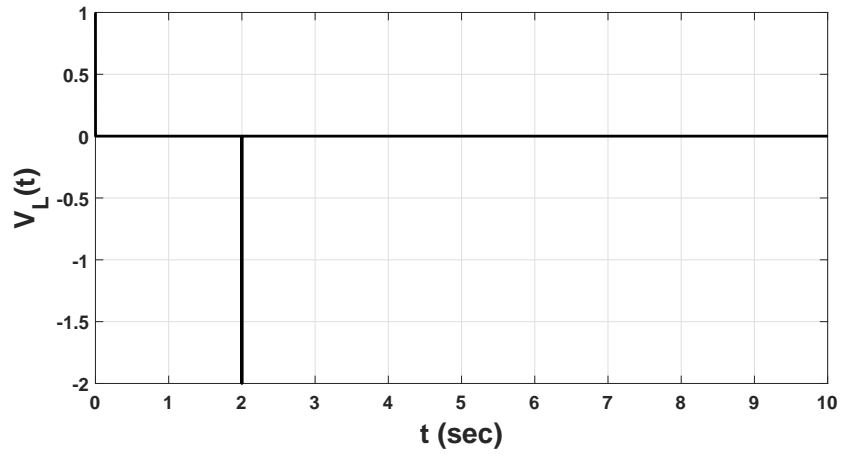


Figure 9

(b)  $i(t) = \delta(t) - 2\delta(t - 1) + \delta(t - 2)$

$V_C(t) = u(t) - 2u(t - 1) + u(t - 2)$

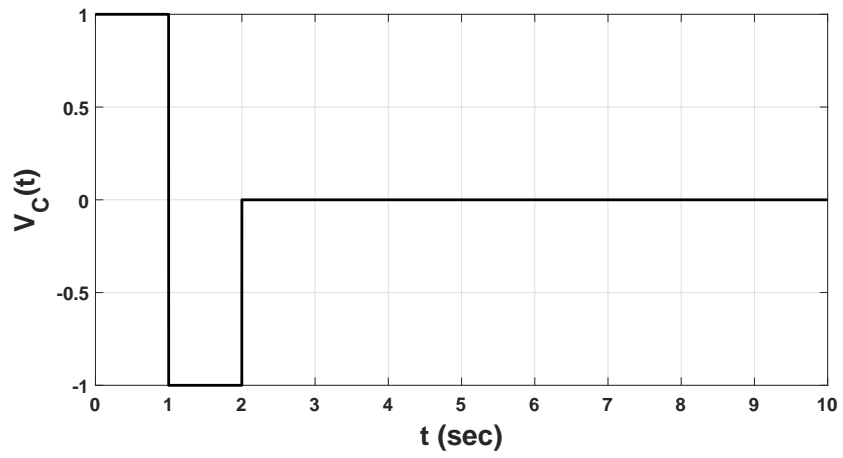


Figure 10

(c)  $i(t) = e^{-2t}u(t)$

$V_C(t) = 0.5(1 - e^{-2t})u(t)$

$V_L(t) = -2e^{-2t}u(t) + \delta(t)$

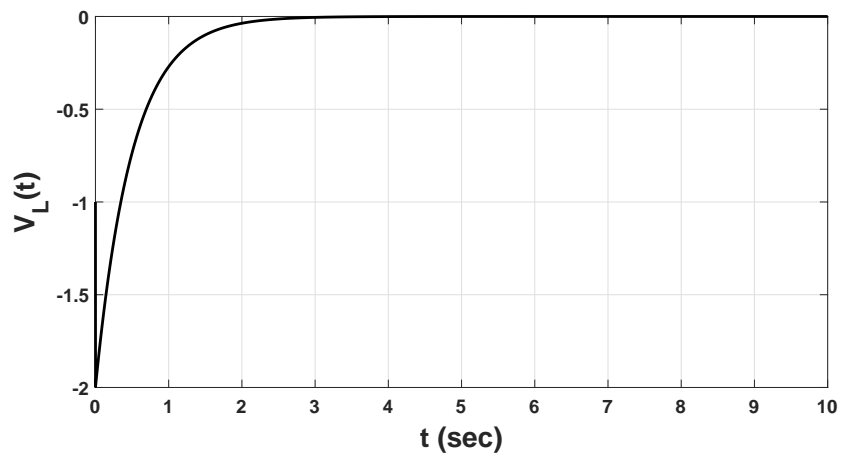


Figure 11

(d)  $\cos(t)u(t)$

$V_C(t) = \sin(t)u(t)$

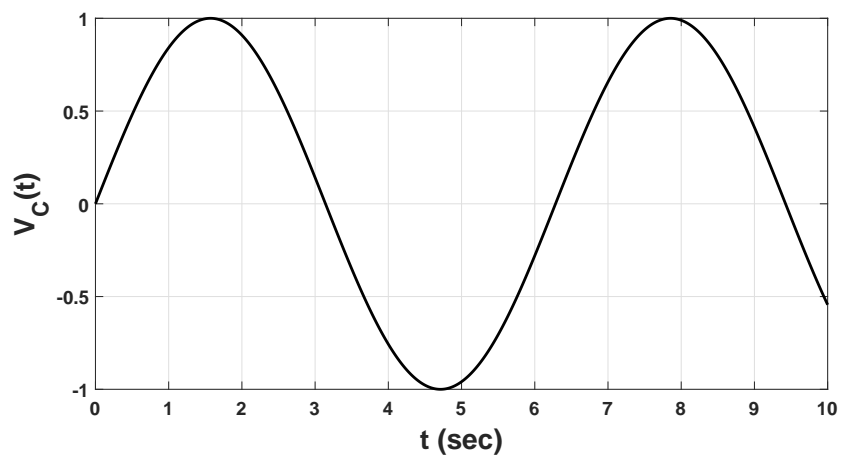


Figure 12

$V_L(t) = -\sin(t)u(t) + \delta(t)$


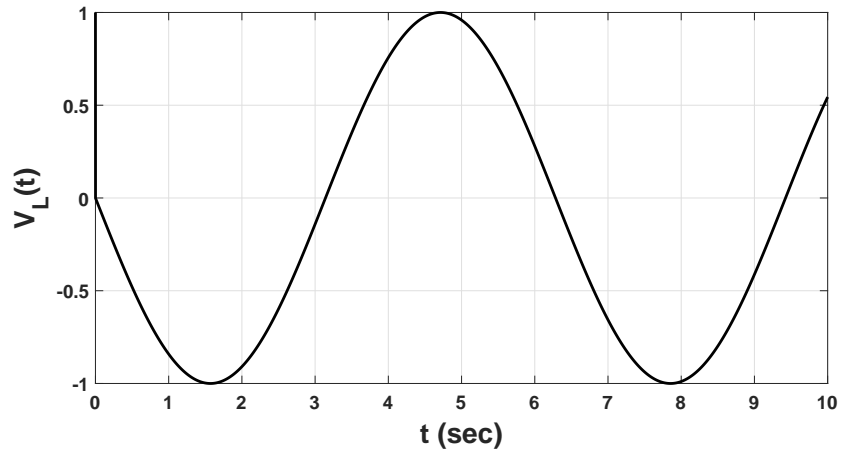
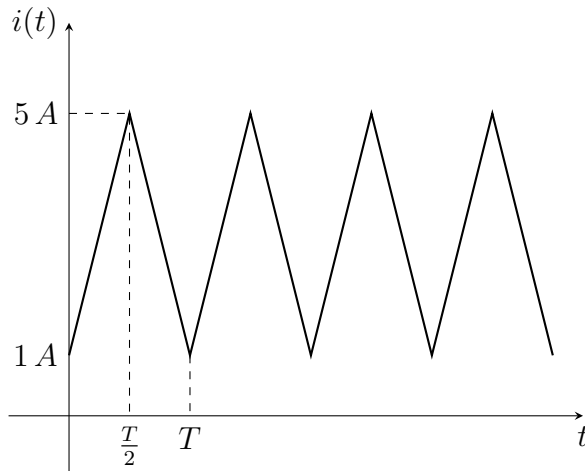


Figure 13

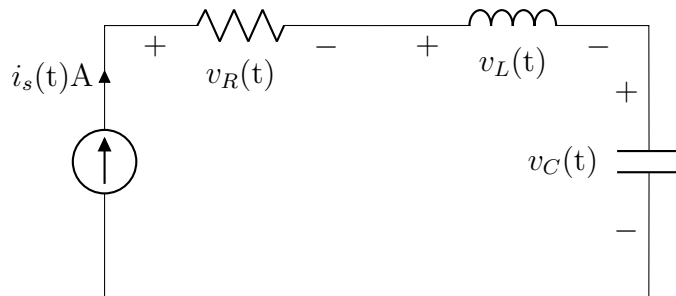6. In the following circuit  $R = 100\Omega$ ,  $L = 1\text{mH}$  and  $C = 1\mu\text{F}$ . Determine the voltages  $v_R(t)$ ,  $v_L(t)$  and  $v_C(t)$  if  $i_s(t)$  is as shown below .




Given waveform is periodic. by considering time period as  $T$  this can be represent as

$$i(t) = u(t) + \frac{8(t - nT)}{T}, \quad nT \leq t \leq nT + \frac{T}{2}$$
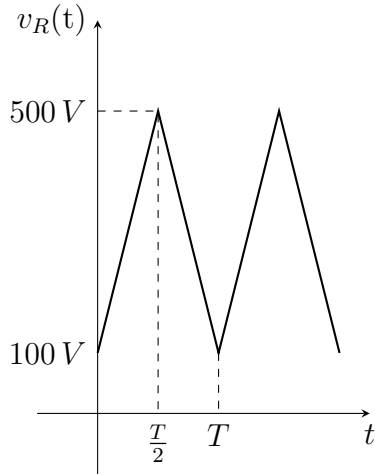
$$= u(t) + 8 - \frac{8(t - nT)}{T}, \quad nT + \frac{T}{2} \leq (n+1)T$$






Current flowing through resistor is equal to source current. therefore voltage across resistor is

$$v_R(t) = 100u(t) + \frac{800(t - nT)}{T}, \quad nT \leq t \leq nT + \frac{T}{2}$$
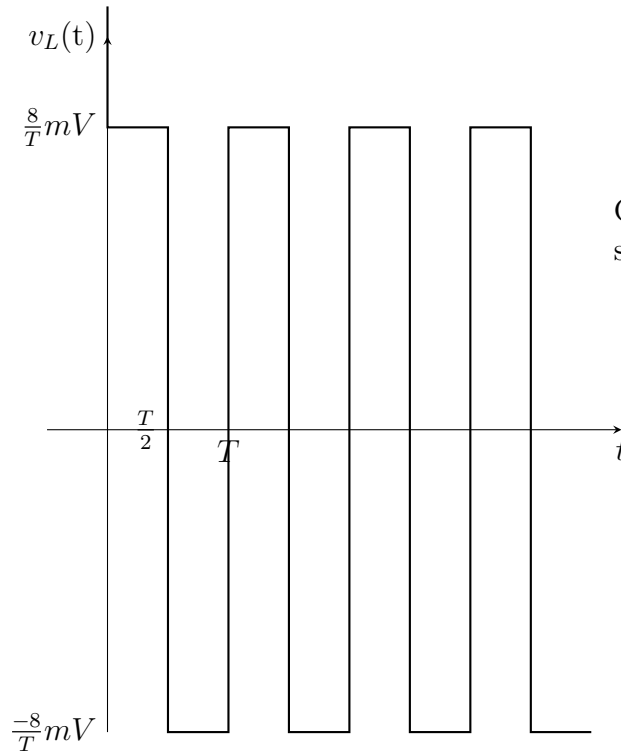
$$= 100u(t) + 800 - \frac{800(t - nT)}{T}, \quad nT + \frac{T}{2} \leq (n+1)T$$




Current flowing through inductor is equal to source current. therefore voltage across inductor is

$$v_L(t) = L \frac{di}{dt}$$

$$= \delta(t) + \frac{8}{T}, \quad nT \leq t \leq nT + \frac{T}{2}$$
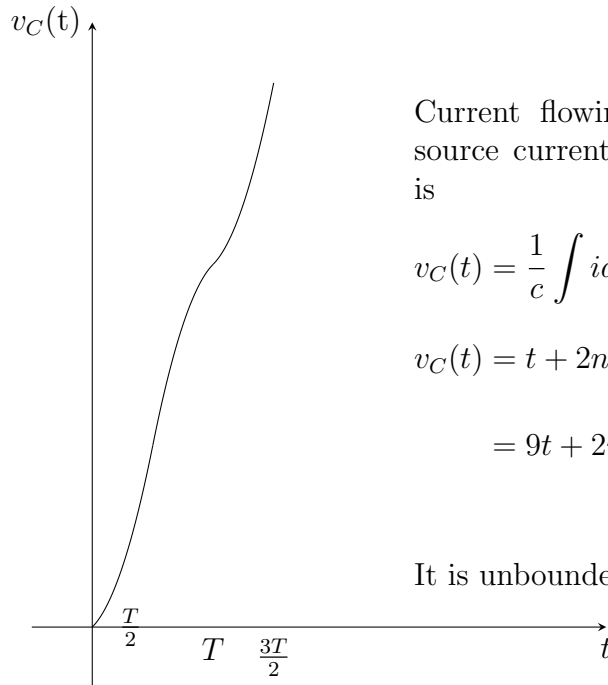
$$= -\frac{8}{T}, \quad nT + \frac{T}{2} \leq (n+1)T$$



Current flowing through capacitor is equal to source current. therefore voltage across capacitor is

$$v_C(t) = \frac{1}{C} \int i dt$$

$$v_C(t) = t + 2nT + \frac{8(\frac{t^2}{2} - nTt)}{T}, \quad nT \leq t \leq nT + \frac{T}{2}$$

$$= 9t + 2nT - \frac{8(\frac{t^2}{2} - nTt)}{T}, \quad nT + \frac{T}{2} \leq (n+1)T$$

It is unbounded.

7. The total inductance ( $L_{eq}$ ) can be calculated in the following way:

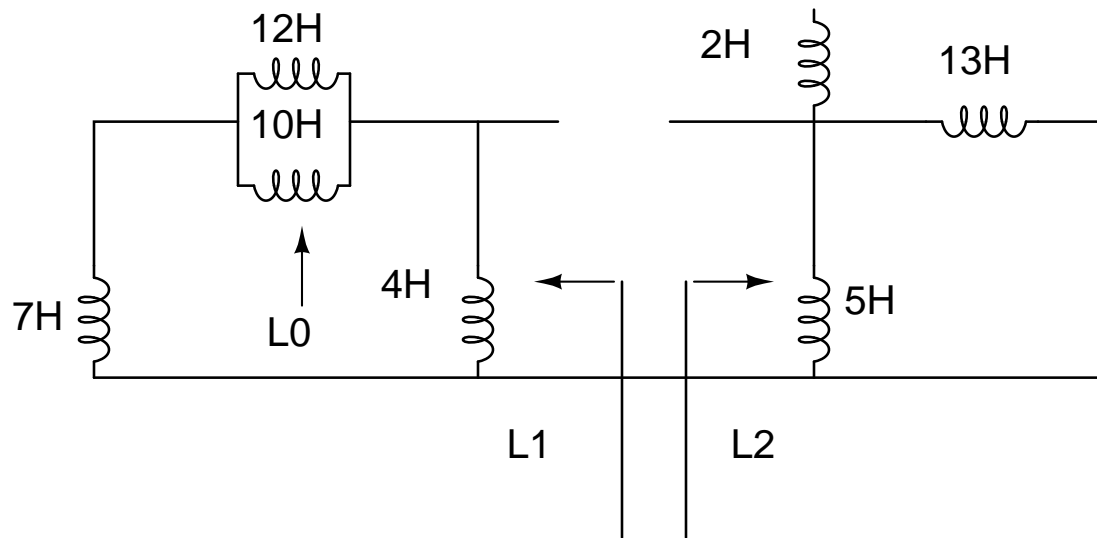


Figure 14: Q 14


$$L0 = \frac{1}{\frac{1}{10} + \frac{1}{12}} = \frac{60}{11} H$$

$$L1 = \frac{1}{\frac{1}{L0+7} + \frac{1}{4}} = \frac{548}{181} H$$


$$L2 = \frac{1}{\frac{1}{5} + \frac{1}{12+1}} = \frac{65}{18} H$$

$$L_{eq} = L1 + L2 = 6.64 H$$

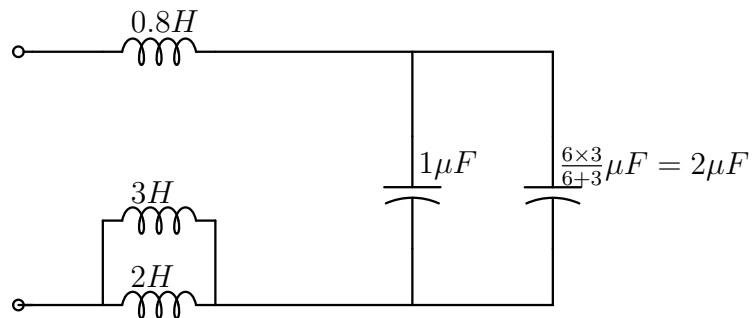
8.  $6\mu F$  and  $3\mu F$  are in series,



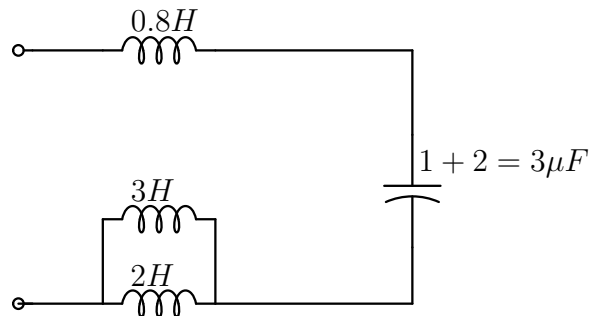
$1\mu F$  and  $2\mu F$  are in parallel,



$2H$ ,  $3H$  are in parallel,

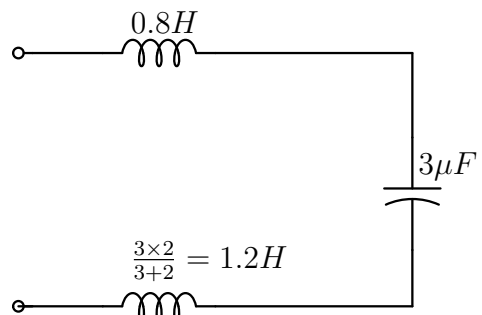

$1.2H$ ,  $0.8H$  are in series

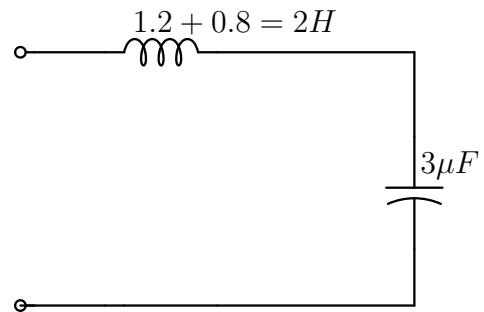


9. a) Applying KCL at the left most node, we get


$$I + i_1 = i_1 + 3I = 3A$$

Applying KVL

$$V = 5V$$

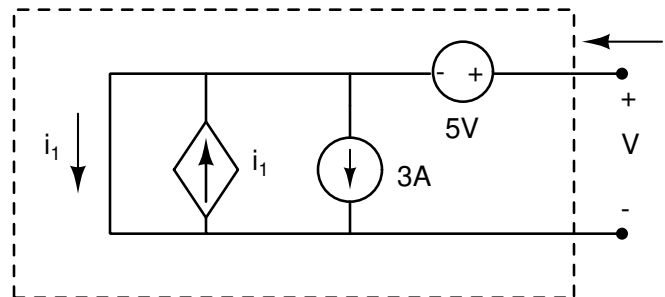


**Figure 15:** Question 9(a)

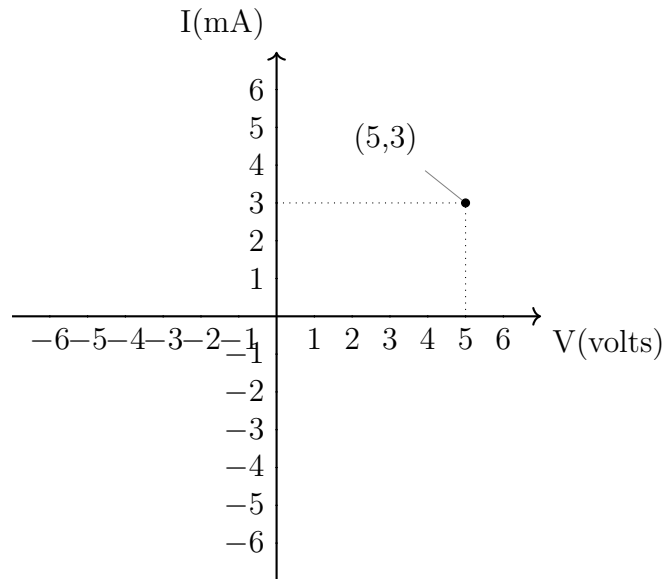

**Figure 16:** I-V characteristics of first box

b) Using KCL

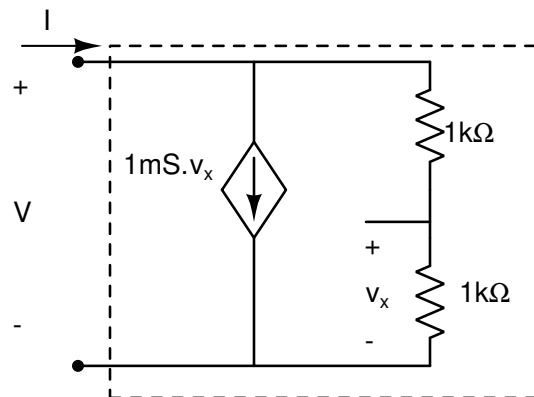


**Figure 17:** Question 9(b)

$$I = \frac{V_x}{1\text{ k}} + \frac{V}{2\text{ k}}$$


Using Ohm's law

$$\begin{aligned} V_2 &= \frac{V}{2\text{ k}} \times 1\text{ k} = \frac{V}{2} \\ I &= \frac{V}{2\text{ k}} + \frac{V}{2\text{ k}} \\ I &= \frac{V}{1\text{ k}} \end{aligned}$$

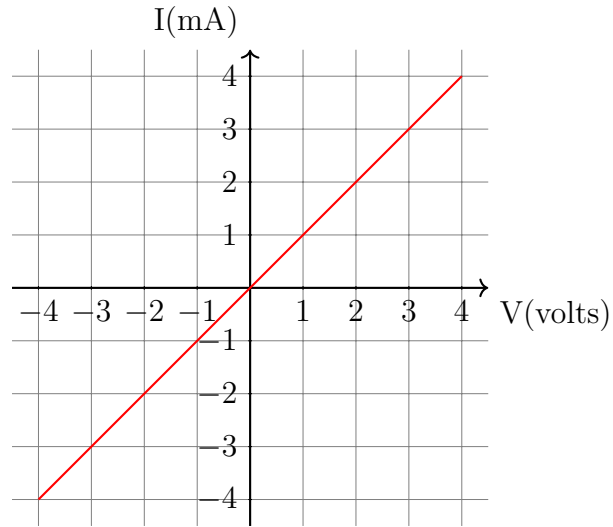

**Figure 18:** I-V characteristics of 2nd box

10. Using KCL and KVL, we get

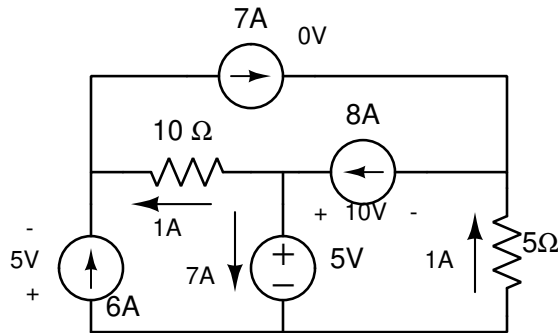

$$P_{5\Omega} = 1^2 \times 5 = 5 \text{ W}; \text{ Dissipated}$$

$$P_{10\Omega} = 1^2 \times 10 = 10 \text{ W}; \text{ Dissipated}$$

$$P_{6A} = 6 \times 5 = 30 \text{ W}; \text{ Absorbs}$$

$$P_{7A} = 7 \times 0 = 0 \text{ W};$$

$$P_{8A} = (-8) \times 10 = -80 \text{ W}; \text{ Delivers}$$

$$P_{5V} = 5 \times 7 = 35 \text{ W}; \text{ Absorbs}$$


For power calculations, the current is positive if it is in the direction of the voltage drop.

11. Let  $V_1$  be the voltage drop across the resistor as shown in the figure. Using Kirchhoff Current

law at the node in the centre

$$\frac{V_1}{4.7} + \frac{V_1}{2.8} + \frac{V_1}{1} + 5 - 3 = 0$$

$$\Rightarrow V_1 = -1.27V$$

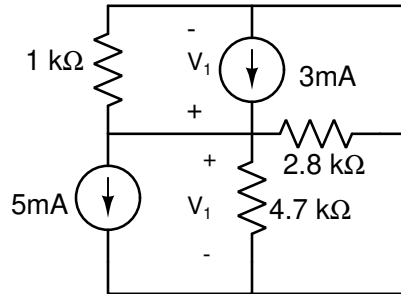

**Figure 19:** Question 3

$$P_{1\text{ k}\Omega} = \frac{(1.27)^2}{1} = 1.61\text{ mW}; \text{Dissipated}$$

$$P_{2.8\text{ k}\Omega} = \frac{(1.27)^2}{2.8} = 0.57\text{ mW}; \text{Dissipated}$$

$$P_{4.7\text{ k}\Omega} = \frac{(1.27)^2}{4.7} = 0.34\text{ mW}; \text{Dissipated}$$


$$P_{3\text{mA}} = V_1 \times (-3) = (-1.27) \times (-3) = 3.81\text{ mW}; \text{Absorbed}$$

$$\Rightarrow \text{Power delivered is } -3.81\text{mW}$$


$$P_{5\text{mA}} = V_1 \times 5 = -6.35\text{ mW}; \text{Generated}$$

$$\Rightarrow \text{Power delivered is } 6.35\text{mW}$$

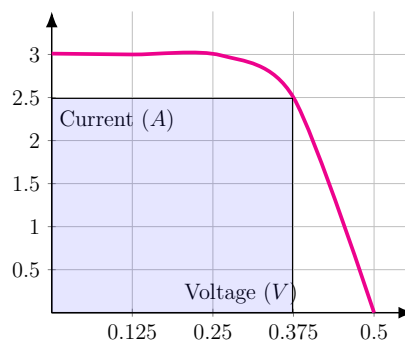12. (a) Short-circuit  $\Rightarrow$  voltage = 0V,  $I(V = 0) = 3A$   
 (b) Open-circuit  $\Rightarrow$  current = 0A,  $V(I = 0) = 0.5V$   
 (c)  $P_{\max} = \text{maximum area under } I-V \text{ curve} = 2.5 \times 0.375 = 0.9375W$



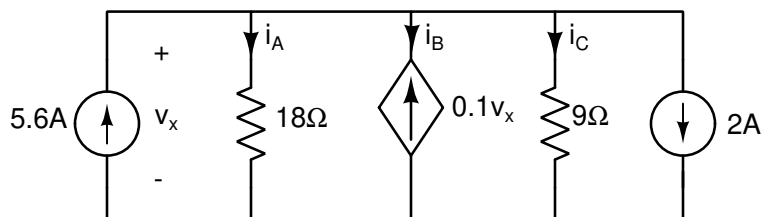
13. Use KCL with  $V_x$  as the branch voltage.



$$\begin{aligned}
 -5.6 + \frac{V_x}{18} - 0.1V_x + \frac{V_x}{9} + 2 &= 0; \\
 \Rightarrow \frac{V_x}{15} &= 3.6; \\
 \Rightarrow V_x &= 54V.
 \end{aligned}$$

$$\begin{aligned}
 \text{Now, } i_a &= \frac{V_x}{18} = 3A; \\
 \text{and, } i_b &= -0.1V_x = -5.4A; \\
 \text{and, } i_c &= \frac{V_x}{9} = 6A.
 \end{aligned}$$

14. Across  $V_\pi$ , resistors  $3\text{ k}\Omega$  and  $15\text{ k}\Omega$  are in parallel,  $3||15 = 2.5\text{ k}\Omega$ .

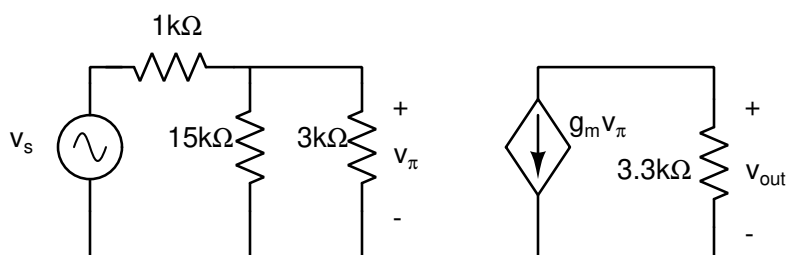

**Figure 20:** Question 6

Using Voltage divider rule:

$$V_\pi = V_s \times \frac{2.5}{2.5 + 1} = \frac{5}{7} V_s$$




Now,  $V_{\text{out}} = -g_m V_\pi \times 3.3k\Omega$

$$\Rightarrow V_{\text{out}} = (-322mS) \times \frac{5}{7} V_s \times 3.3k\Omega$$

$$\Rightarrow V_{\text{out}} = -759 \times V_s$$

$$\Rightarrow V_{\text{out}} = -759 \times (6 \cos 2300t \mu V)$$
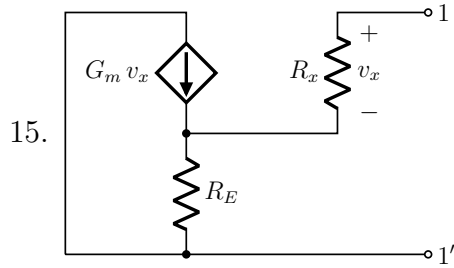
$$\Rightarrow V_{\text{out}} = -4554 \cos 2300t \mu V = -4.554 \cos 2300t mV$$



If we connect, a current source with  $I = 1A$  between terminals 1 and 1',


$$v_x = R_x \quad (1)$$

Current through  $R_E$ ,  $I_{R_E} = G_m v_x + \frac{v_x}{R_x}$   
Voltage across  $R_E$ ,  $V_{R_E} =$


$$\left( G_m + \frac{1}{R_x} \right) R_E v_x$$

$$V_{11'} = V_{R_E} + v_x = R_x + (1 + G_m R_x) R_E \quad (\because \text{From (1)})$$

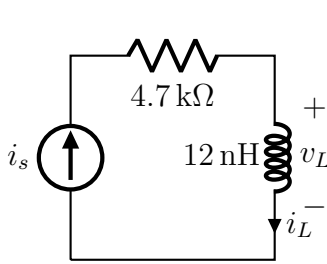
$$R_{\text{eq}} = V_{11'} = 230 k\Omega \quad (\because I_{11'} = 1A)$$




(i)

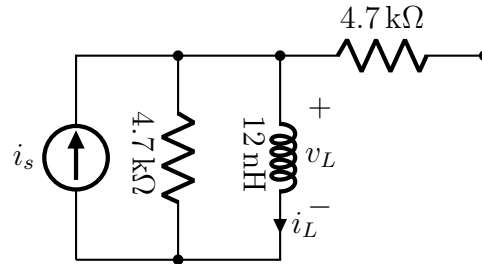


(ii)

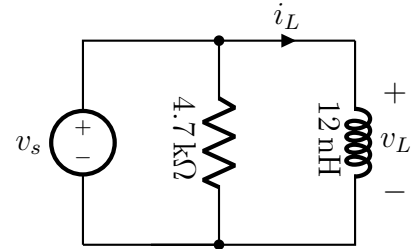


(iii)

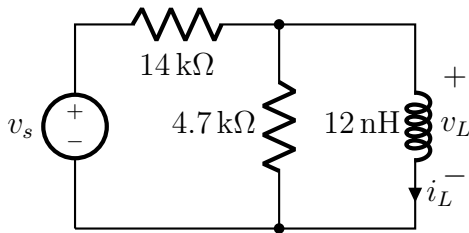

(iv)

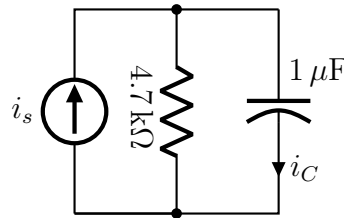

(v)

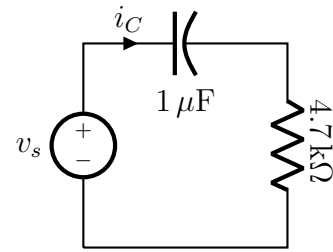

(vi)

16. (a) In steady state,  $v_L = 0$  and  $i_C = 0$

(i)  $i_s = i_L = 1mA$

(ii)  $i_L = 1mA$

(iii) Circuit does not reach steady-state,  $i_L$  is indeterminate

(iv)  $i_L = \frac{2}{14000} = \frac{1}{7} mA$

(v) and (vi)  $i_C = 0$