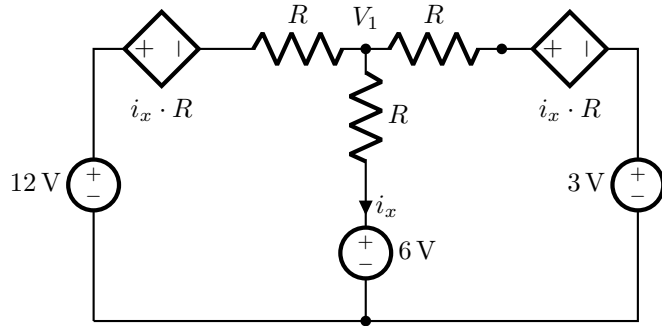


Tutorial 2

August 16, 2024


1.



$$\begin{aligned} \frac{12 - 10ki_x - V_1}{10k} + \frac{3 + 10ki_x - V_1}{10k} &= \frac{V_1 - 6}{10k} \\ 15 - 2V_1 &= V_1 - 6 \\ \Rightarrow V_1 &= 7V \\ i_x &= \frac{V_1 - 6}{10} mA \\ i_x &= \frac{1}{10} mA \end{aligned}$$

Power absorbed by the 6V source = $6 \times i_x = 6 \times 0.1 = 0.6mW$
 Power delivered = $-0.6mW$

2.

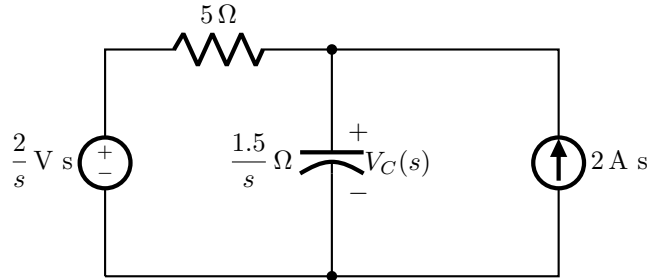

(a) Applying KCL at the capacitor node,


$$\begin{aligned} \frac{V_C(s) - \frac{2}{s}}{5} + \frac{V_C(s)}{\frac{1.5}{s}} - 2 &= 0 \\ \frac{V_C(s)s - 2}{5s} + \frac{V_C(s)s}{1.5} &= 2 \\ \frac{1.5V_C(s)s - 3 + 5V_C(s)s^2}{7.5s} &= 2 \\ 1.5V_C(s)s - 3 + 5V_C(s)s^2 &= 15s \\ V_C(s) \times 5s(s + 0.3) &= 5s(3s + 0.6) \\ V_C(s) &= \frac{3s + 0.6}{s(s + 0.3)} \end{aligned}$$

split into partial fractions


$$V_C(s) = \frac{2}{s} + \frac{1}{s + 0.3}$$

(b) $v_C(t) = \mathcal{L}^{-1}(V_C(s)) = 2u(t) + e^{-0.3t}u(t)$

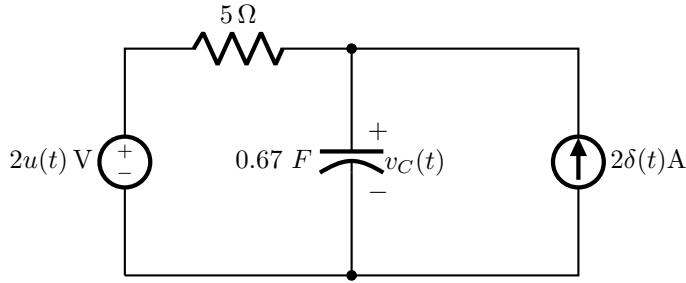(c) time-domain representation of the circuit,




3. To find $Z(s)$:

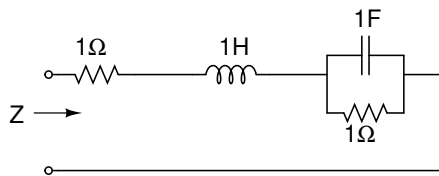


$$\begin{aligned} Z(s) &= 1 + s + \left(\frac{1}{s} \parallel 1 \right) \\ &= 1 + s + \frac{\frac{1}{s} \times 1}{1 + \frac{1}{s}} \\ &= 1 + s + \frac{1}{s+1} \\ &= \frac{s^2 + 2s + 2}{s+1} \end{aligned}$$

4. To find $Y(s)$:

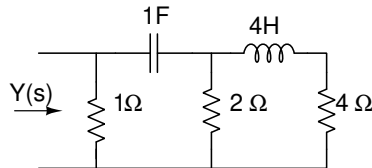

$$\begin{aligned} Z(s) &= 1 \parallel \left(\frac{1}{s} + 2 \parallel (4s + 4) \right) \\ &= 1 \parallel \left(\frac{1}{s} + \frac{2 \times 4(s+1)}{(2 + 4s + 4)} \right) \\ &= 1 \parallel \left(\frac{1}{s} + \frac{8(s+1)}{(4s+6)} \right) \\ &= 1 \parallel \left(\frac{4s+6+8s^2+8s}{(4s^2+6s)} \right) \\ &= \frac{\frac{(8s^2+12s+6)}{(4s^2+6s)} \times 1}{1 + \frac{(8s^2+12s+6)}{(4s^2+6s)}} \\ &= \frac{(8s^2+12s+6)}{(4s^2+6s+8s^2+12s+6)} \\ &= \frac{(8s^2+12s+6)}{(12s^2+18s+6)} \\ \Rightarrow Y(s) &= \frac{1}{Z(s)} \\ &= \frac{(12s^2+18s+6)}{(8s^2+12s+6)} \\ &= \frac{(6s^2+9s+3)}{(4s^2+6s+3)} \end{aligned}$$

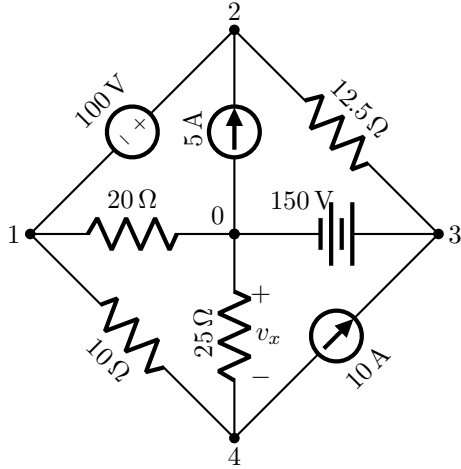5. Nodal analysis: Assume that the current through the 100V source from node 1 to node 2 is i_1 . The voltage at node 3 is known; need not write an equation at this node. The nodal equations at nodes 1, 2 and 4 can be written as follows.



$$-i_1 + \frac{V_1}{20} + \frac{V_1 - V_4}{10} = 0 \quad (1)$$

$$i_1 - 5 + \frac{V_2 - 150}{12.5} = 0 \quad (2)$$

Adding equations (1) and (2), we get

$$\frac{V_1}{20} - 5 + \frac{V_1 - V_4}{10} + \frac{V_2 - 150}{12.5} = 0 \quad (3)$$

$$\frac{V_4 - V_1}{10} + \frac{V_4}{25} + 10 = 0 \quad (4)$$

$$V_2 - V_1 = 100V \quad (5)$$

Arranging equations (3), (4) and (5) in matrix form,

$$\begin{pmatrix} -1 & 1 & 0 \\ 10 & 0 & -14 \\ 15 & 8 & -10 \end{pmatrix} \cdot \begin{pmatrix} V_1 \\ V_2 \\ V_4 \end{pmatrix} = \begin{pmatrix} 100 \\ 1000 \\ 1700 \end{pmatrix}$$

$$V_1 = 11.71 \text{ V}, V_2 = 111.71 \text{ V}, V_3 = 150 \text{ V}, V_4 = -63.06 \text{ V}$$

$$v_x = -V_4 = 63.06 \text{ V}$$

6. Using the circuit model, we have

$$v_{ab} = \frac{1M\Omega}{1M\Omega + 500\Omega} \times 200mV = 199.9mV$$

$$\text{Input voltage to the speaker} = 120v_{ab} = 23.988V$$


By applying voltage division rule across speaker resistor,

$$16 = \frac{10}{10 + R} \times 23.988$$

$$\Rightarrow R = 4.9925\Omega \approx 5\Omega$$

Power delivered to the speaker,
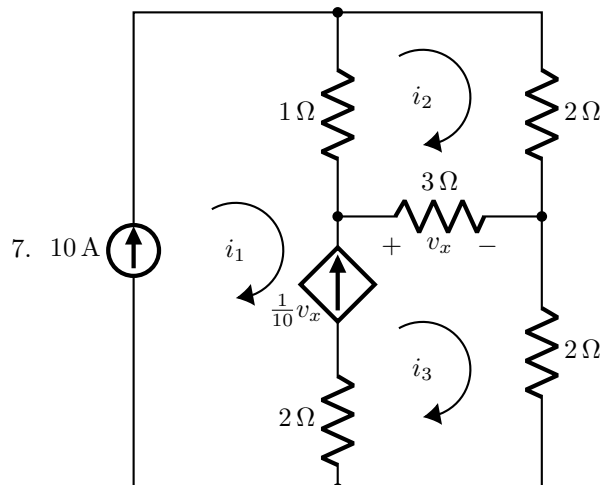
$$P_D = \frac{V^2}{R} = \frac{16^2}{10} = 25.6W$$



$$\text{Clearly, } i_1 = 10A \quad (1)$$

$$\text{and } i_3 - i_1 = \frac{v_x}{10}$$

$$\text{where } v_x = 3(i_3 - i_2)$$

$$\Rightarrow 0.7i_3 + 0.3i_2 = 10 \quad (2)$$

Using KVL for mesh (2)

$$2i_2 + 3(i_2 - i_3) + 1(i_2 - i_1) = 0 \quad (3)$$

From (2) and (3),

$$6i_2 - 3i_3 = 10$$

$$0.3i_2 + 0.7i_3 = 10$$

Solve for i_2 and i_3 to get, $i_2 = 7.2549 \text{ A}$, $i_3 = 11.1765 \text{ A}$

8. Since the current through the 2Ω resistor is $\frac{2}{s}$, we need to write the nodal equations only at nodes 2 and 3. V_1 can be obtained as $V_2 + 100\frac{2}{s}$. Similarly $V_4 = V_3 - 2\frac{5}{s}$.

$$\frac{-2}{s} + V_2 \left(1 + \frac{s}{5}\right) - V_3 \cdot \frac{s}{5} = 0 \quad (1)$$

$$\frac{s}{5}(V_3 - V_2) + \frac{V_3}{2s} + \frac{s}{5} = 0 \quad (2)$$


Using equations (1) and (2), we have

$$\begin{pmatrix} 1 + \frac{s}{5} & -\frac{s}{5} \\ -\frac{s}{5} & (\frac{1}{2s} + \frac{s}{5}) \end{pmatrix} \begin{pmatrix} V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} \frac{2}{s} \\ -\frac{s}{5} \end{pmatrix}$$

$$V_2(s) = -\frac{6s^2 - 10}{s(2s^2 + s + 5)} \longleftrightarrow v_2(t) = 2u(t) - 5e^{-t/4} \left[\cos\left(\frac{\sqrt{39}}{4}t\right) - \frac{\sqrt{39}}{195} \sin\left(\frac{\sqrt{39}}{4}t\right) \right] u(t) \text{ V}$$

$$V_3(s) = -\frac{6s + 50}{2s^2 + s + 5} \longleftrightarrow v_3(t) = -3e^{-t/4} \left[\cos\left(\frac{\sqrt{39}}{4}t\right) + \frac{97\sqrt{39}}{117} \sin\left(\frac{\sqrt{39}}{4}t\right) \right] u(t) \text{ V}$$

9. s-domain representation of circuit,

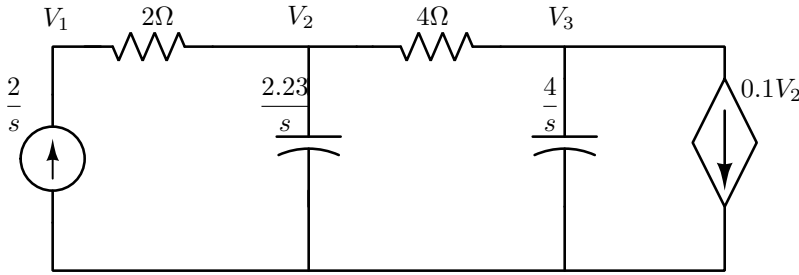

Once again write equations only for V_2 and V_3 .

$$V_2 \cdot 0.45s + \frac{V_2 - V_3}{4} = \frac{2}{s} \quad (1)$$

$$\frac{V_3 - V_2}{4} + V_3 \cdot \frac{s}{4} + 0.1V_2 = 0 \quad (2)$$

$$\begin{pmatrix} (0.45s + 0.25) & -0.25 \\ -0.15 & 0.25(1 + s) \end{pmatrix} \cdot \begin{pmatrix} V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} \frac{2}{s} \\ 0 \end{pmatrix}$$

$$\Rightarrow \begin{pmatrix} V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} \frac{0.5(s+1)}{s(0.1125s^2 + 0.175s + 0.025)} \\ \frac{-0.3}{s(0.1125s^2 + 0.175s + 0.025)} \end{pmatrix}$$

Expanding using partial fractions, we get

$$V_2(s) = \frac{22.53}{s} + \frac{136.32}{(s + 0.159)} - \frac{158.85}{(s + 0.1396)} \longleftrightarrow v_2(t) = 22.53u(t) + 136.32e^{-0.159t}u(t) - 158.85e^{-0.1396t}u(t)$$

$$V_3(s) = \frac{-13.51}{s} - \frac{97.26}{(s + 0.159)} + \frac{110.77}{(s + 0.1396)} \longleftrightarrow v_3(t) = -13.52u(t) - 97.26e^{-0.159t}u(t) + 110.78e^{-0.1396t}u(t)$$