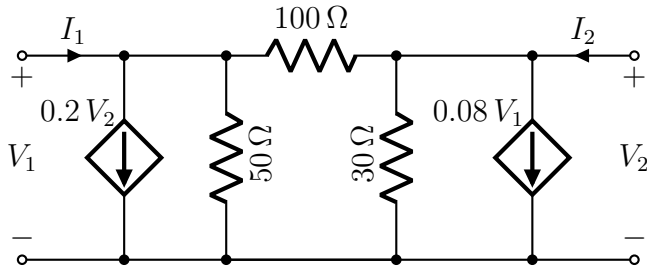


# EE2015: Electric Circuits and Networks

## Tutorial 4

(September 6, 2024)


1.




Obtain the impedance and admittance parameters for the two-port network shown on the left.

2. (a) Find the  $h$ -parameters of the two-port network shown below.

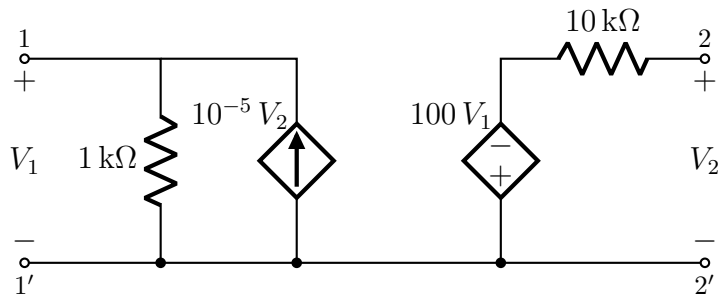(b) Find  $\mathbf{Z}_{\text{out}}$  if an input  $\mathbf{V}_s$  having source resistance of  $R_s = 200\ \Omega$  is connected at 11'.



3.

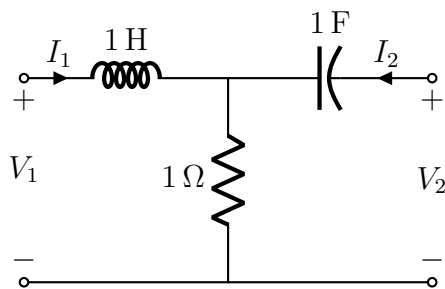

Consider the two-port network shown on the left. Find its  $g$ -parameters.


4. Find the  $z$  and  $g$  parameters of a network if the T parameters are

$$T = \begin{bmatrix} 10 & 1.5\Omega \\ 2S & 4 \end{bmatrix}$$

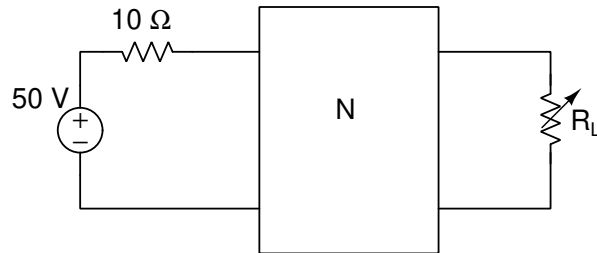
5. The T parameters of the network  $N$  in the figure below are

$$T = \begin{bmatrix} 10 & 1.5\Omega \\ 2S & 4 \end{bmatrix}$$


The output port is connected to a variable load resistor  $R_L$ . Find  $R_L$  for maximum power transfer. What is the maximum power transferred?



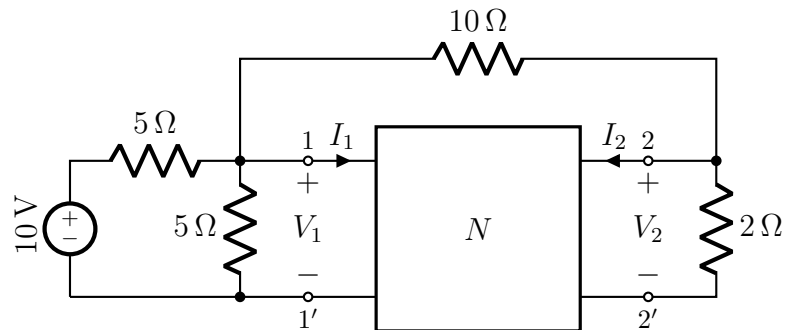6. A resistive symmetric two-port network  $N$  is shown on the right. It was observed that  $y_{11} = 0.2\text{ S}$  and  $y_{12} = -0.05\text{ S}$ . Find the port voltages.



- 7.

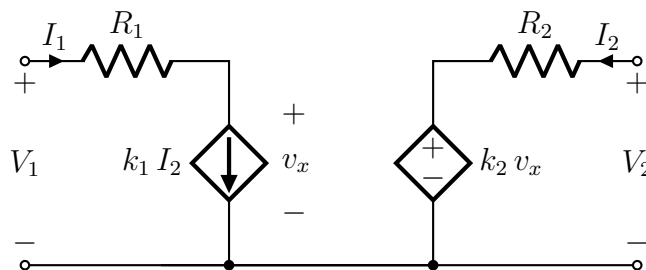

Consider the two-port network shown on the left. Find the condition that  $k_1$ ,  $k_2$ ,  $R_1$ , and  $R_2$  should satisfy for the network to be reciprocal.

8. Consider the resistive two-port network  $N$  shown below on the left. When an independent source of  $10\text{ V}$  was connected as shown, the measured voltage at port 2 was  $2\text{ V}$ . The same network  $N$  is now connected in the configuration shown on the right. Find the power dissipated in  $R_x$  in this configuration.

